
ELEC 402

Standard Cell Layout **Lecture 10**


Reza Molavi
Dept. of ECE
University of British Columbia
reza@ece.ubc.ca

Slides Courtesy : Prof. Sudip Shekhar (UBC)




Gate Layout

- Layout can be very time consuming
 - Design gates to fit together nicely
 - Build a library of standard cells
 - Use PNR (placement & routing) tools for synthesis
- Standard cell design methodology
 - V_{DD} and GND should abut (standard height)
 - Adjacent gates should satisfy design rules so as to “snap together”
 - NMOS at bottom and PMOS at top
 - All gates include well and substrate contacts
 - Use poly and M1 to route the standard cells and leave upper metal layers (M2, M3...) as routing channels to interconnect cells
 - Upper metal layers often follow HVH or VHV track direction to ease PNR

 


Standard Cells – Inverter

 


Pitch = repetitive distance between objects
 Metal track is $\sim 6\lambda$ pitch (3λ width + 3λ space)
 Cell height 12 metal tracks (integer # tracks)
 Cell height is "12 pitch"

Rails $\sim 10\lambda$

 


- Horizontal N-diffusion and P-diffusion strips, Vertical polysilicon gates
- Metal1 V_{DD} and GND rails at top and bottom respectively
- $\lambda = 0.125 \mu\text{m}$ in $0.25 \mu\text{m}$ process \rightarrow not that useful in newer technologies


Standard Cells – NAND2

 

2-input NAND gate

 


A simple Standard Cell Library

 

45 nm GPDK we use for class projects may have different gate layout


Standard Cell Layout Methodology

 

➤ **Contacts & Wells not shown**

Pitch Matching of Snap-Together Cells

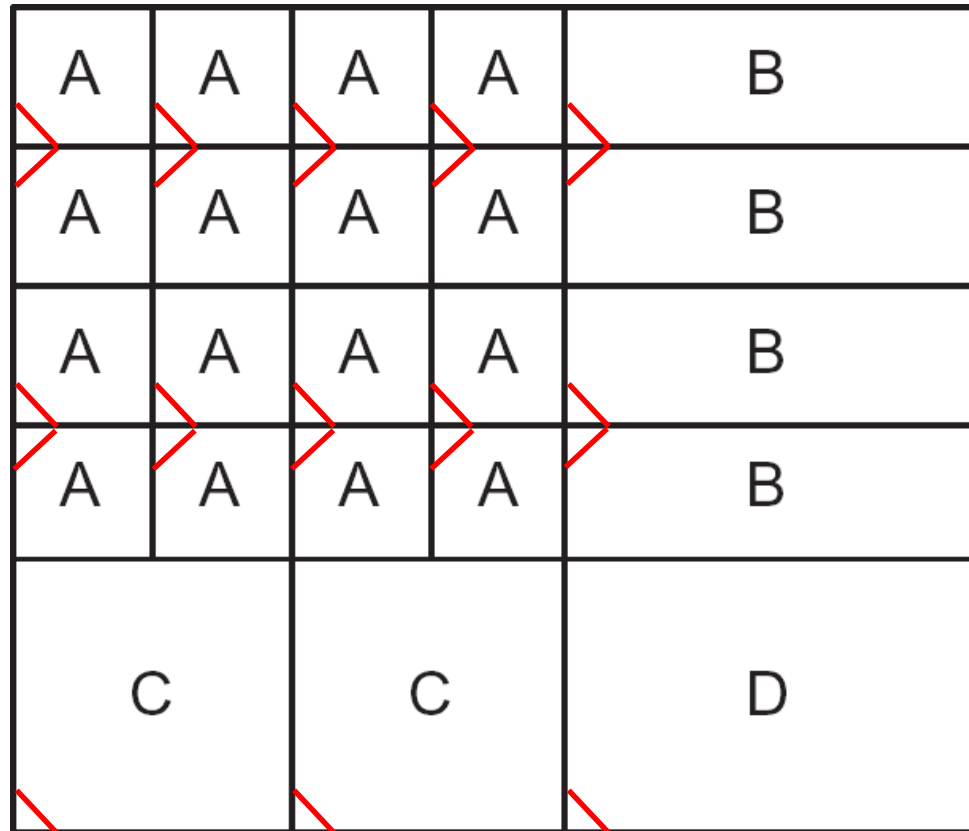The two technique allowing to repeat structures and abut them together




➤ **Stepping**

Pitch matching is a necessity

Pitch Matching of Snap-Together Cells

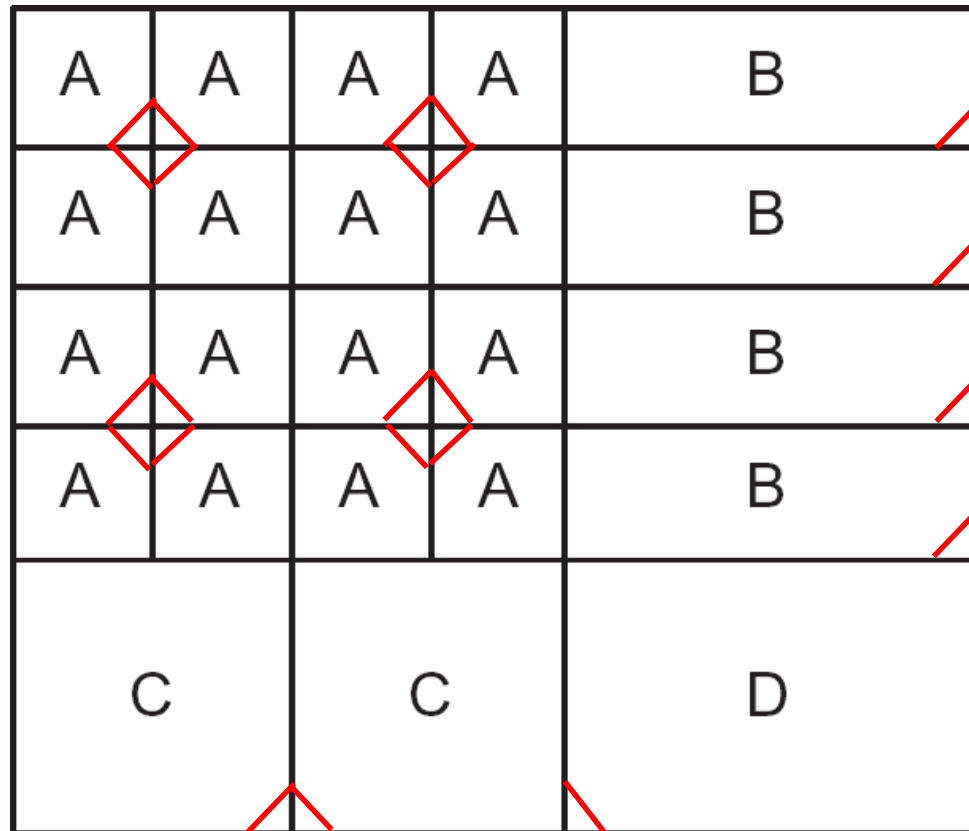The two technique allowing to repeat structures and abut them together




➤ **Flipping**


Pitch matching is a necessity

Multi-Fingered Transistors

One finger

 

Two fingers (folded)

 


Less diffusion capacitance


- For a very wide transistor that does not fit in the standard cell height, break the transistor into multiple fingers → wide layout

Stick Diagrams

 - Contains no dimensions
- Represents relative positions of transistors
- Help plan layout quickly



INV

 

NAND3


- metal1
- poly
- ndiff
- pdiff
- contact

Stick Diagrams Example: 03AI


The goal is to draw the layout such that

 1. there is no discontinuity in diffusion areas
2. gates (polysilicon in red) run vertically
3. No need for crossovers

M1 (first metal layer) is drawn in blue to make necessary connections





Two Possibilities

 

- Line of diffusion layout – abutting source-drain connections
- Crossover eliminated by A B C ordering


Stick Diagrams & Logic Graph

  

- Systematic approach to derive order of input signal wires so gate can be laid out to minimize area
- PU and PD are duals (parallel \leftrightarrow series)
- Vertices are nodes (signals) of circuit, VDD, X, GND; Edges are transistors



Consistent Euler Trail

 - A B C
- C A B
- B C A → no PD
- B A C
- A C B → no PD
- C B A




- A path through all nodes in the graph such that each edge is visited once and only once.
- The sequence of signals on the path is the signal ordering for the inputs.
- PU and PD Euler paths are (must be) consistent (same sequence)
- If you can define a Euler path then you can generate a layout with no diffusion breaks

Logic Graph: OAI22

  


Stick Diagram


Example 2: AOI22 $x = (ab+cd)'$

 

 (a) Logic graphs for $\overline{(ab+cd)}$





(b) Euler Paths $\{a b c d\}$

 




(c) stick diagram for ordering $\{a b c d\}$

Circuit Diagram

Example 2: $Y = (ab+c+d)'$

  

NAND3 with Good Layout

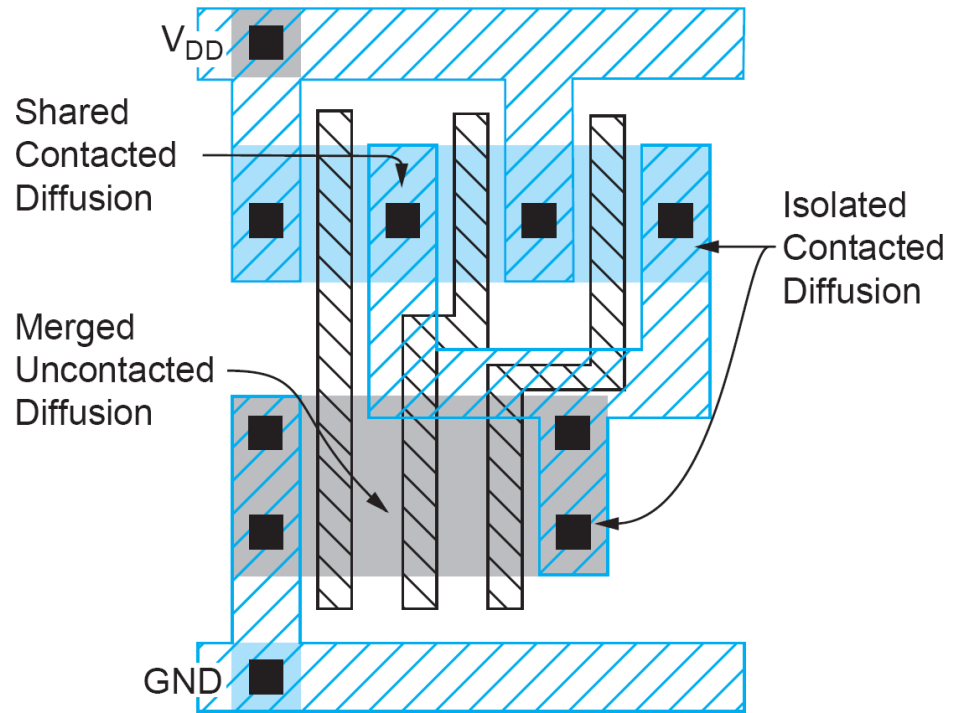  

Actual diffusion cap on the output is 7C, instead of 9C

Example Key

$$\text{Out}' = a(d+e) + bc$$

