

---

# ELEC 402


## Delay in CMOS circuit Lecture 8

Reza Molavi  
Dept. of ECE  
University of British Columbia  
reza@ece.ubc.ca

Slides Courtesy : Dr. Res Saleh (UBC), Dr. Sudip Shekhar (UBC)

---

# Different Delay Definitions

 

“Delay”  $\rightarrow t_{pd}$

Max-time  $\rightarrow$  Propagation time

Min-time  $\rightarrow$  Contamination time

**Rise Time ( $t_r$ ,  $t_{LH}$ ):** time taken to rise from 10% to 90% (sometimes 20% to 80%) **Fall Time ( $t_f$ ,  $t_{HL}$ ):** time taken to drop from 90% to 10% (sometimes 80% to 20%) **Edge Rate ( $t_{rf}$ ):**  $(t_r + t_f)/2$ .

**Rise propagation delay ( $t_{pdr}$ ,  $t_{pLH}$ ):** maximum time from the input crossing 50% to output crossing 50%, with output rising





**Fall propagation delay ( $t_{pdf}$ ,  $t_{pHL}$ ):** maximum time from the input crossing 50% to output crossing 50%, with output falling

**Propagation Delay ( $t_{pd}$ ):**  $(t_{pHL} + t_{pLH})/2$ .

**Contamination Delay ( $t_{cd}$ ):** minimum time from the input crossing 50% to the output crossing 50%.
    
# Inverter – Sizing

- In ratioed logic families (such as diode-connected load or pseudo NMOS,  $V_{OL}$  is a priority so the Size of load is mainly determined by the choice of  $V_{OL}$
- In non-ratioed logic families (such CMOS inverters) propagation delay is important




Pull-down (output capacitor discharge)  
through the NMOS transistor

$$V_{out}(t) = V_{DD} e^{-t/R_N C_L}$$

$T_{PHL}$  is the time it take for the capacitor to discharge to 50% of the final value

(Board notes)


# Effective Resistance Calculations

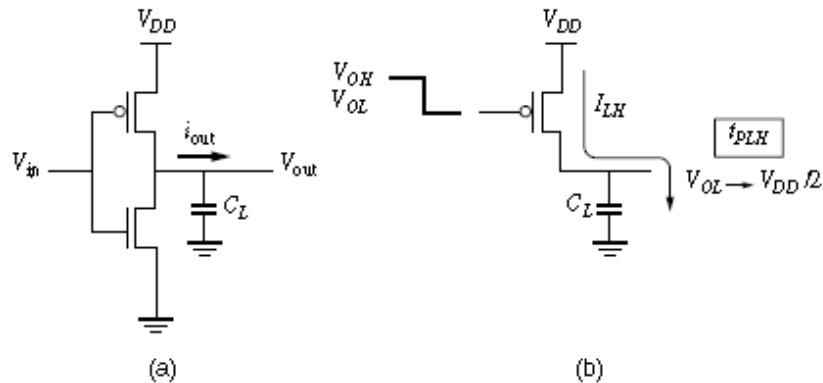

Calculate the delay from the charge/discharge of capacitor

$$I = C_L \frac{dV}{dt} \rightarrow \Delta t \approx \frac{C_L \Delta V}{I_{DS}}$$
 
$$t_{PHL} = \frac{C_L (V_{DD}/2)}{I_{HL}}$$



Assuming **45 nm process**:  $V_{DD} = 1 \text{ V}$ ,  $V_T = 0.35 \text{ V}$ , and  $E_C L = 0.3 \text{ V}$

$$V_{dsat} = \frac{(1-0.35)(0.3)}{(1-0.35+0.3)} \sim 0.2 \text{ V}$$

Since for  $T_{PHL}$   $V_{out}$  changes from  $V_{DD}$  to  $V_{DD}/2$   $\Rightarrow$   $t_{PHL} = \frac{C_L (V_{DD}/2)}{(I_{Dsat})_n}$   $R_N = \frac{V_{DD}/2}{0.7(I_{Dsat})_n}$

NMOS remains in Saturation throughout  $T_{PHL}$ , i.e.  $I_{HL} = I_{dsat}$  equivalent resistance

# Inverter – Resistance

- The value of  $T_{PHL}$  or  $T_{PLH}$  determine the value of the resistor (average on-resistance)
- Note that in the pull-down case (NMOS on) device starts in saturation ( $V_{DD}$  across its  $V_{DS}$  and might enter triode at some point, therefore it makes sense to define an effective resistance
- This **effective resistance** is inversely proportional to  $W/L$  for long channel devices (motivates a  $R_{\square}$  value) while it is inversely proportional to  $W$  in short channel devices (motivates a  $k\Omega \cdot \mu m$  number for transistors)

**45 nm**

**130 nm**

$$R_n = R_{n\_unit} / W$$

$$R_N = R_{eqn} \times \frac{L_N}{W_N}$$

$$R_p = R_{p\_unit} / W$$

$$R_P = R_{eqp} \times \frac{L_P}{W_P}$$

$$R_{n\_unit} = 34 \text{ k}\Omega \cdot \mu m$$


$$R_{eqn} = 12.5 \text{ k}\Omega / \square$$

$$R_{p\_unit} = 68 \text{ k}\Omega \cdot \mu m$$


$$R_{eqp} = 30 \text{ k}\Omega / \square$$

note the ration 2 or 2.4 between NMOS and PMOS, does this remind you of a Particular property?

# Inverter- Capacitances

 


One inverter driving another

 

Showing all capacitances

 Capacitance relevant for delay calculation, i.e.  
Sum of all capacitance at the output of first inverter




# Equivalent Circuits for Transistors

- MOS transistor == Ideal switch + cap and ON resistance
- Unit nMOS has res  $R$ , cap  $C$
- Unit pMOS has res  $2R$ , cap  $C$
- Cap proportional to width
- Res inversely proportional to width
- Some capacitances may be shorted!


- Capacitance

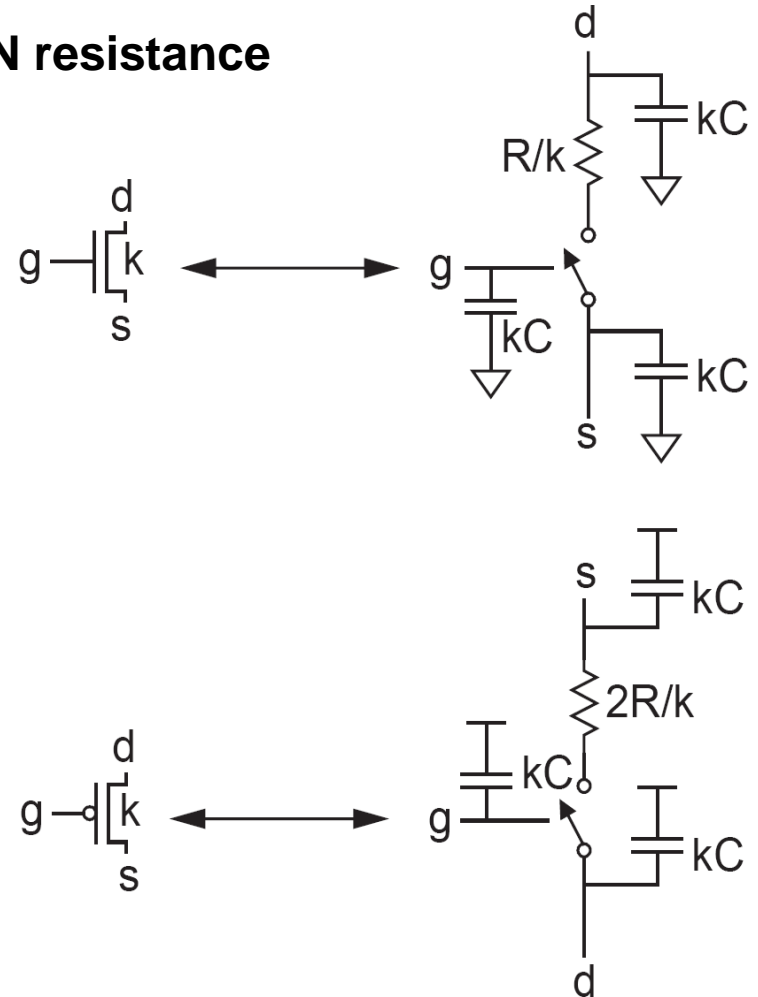- $C = C_g = C_s = C_d = 2 \text{ fF}/\mu\text{m}$  of gate width before 65 nm
- Gradually decline to  $1 \text{ fF}/\mu\text{m}$  in 65 nm and below



# Load Capacitance Calculations

## "Self Capacitance"

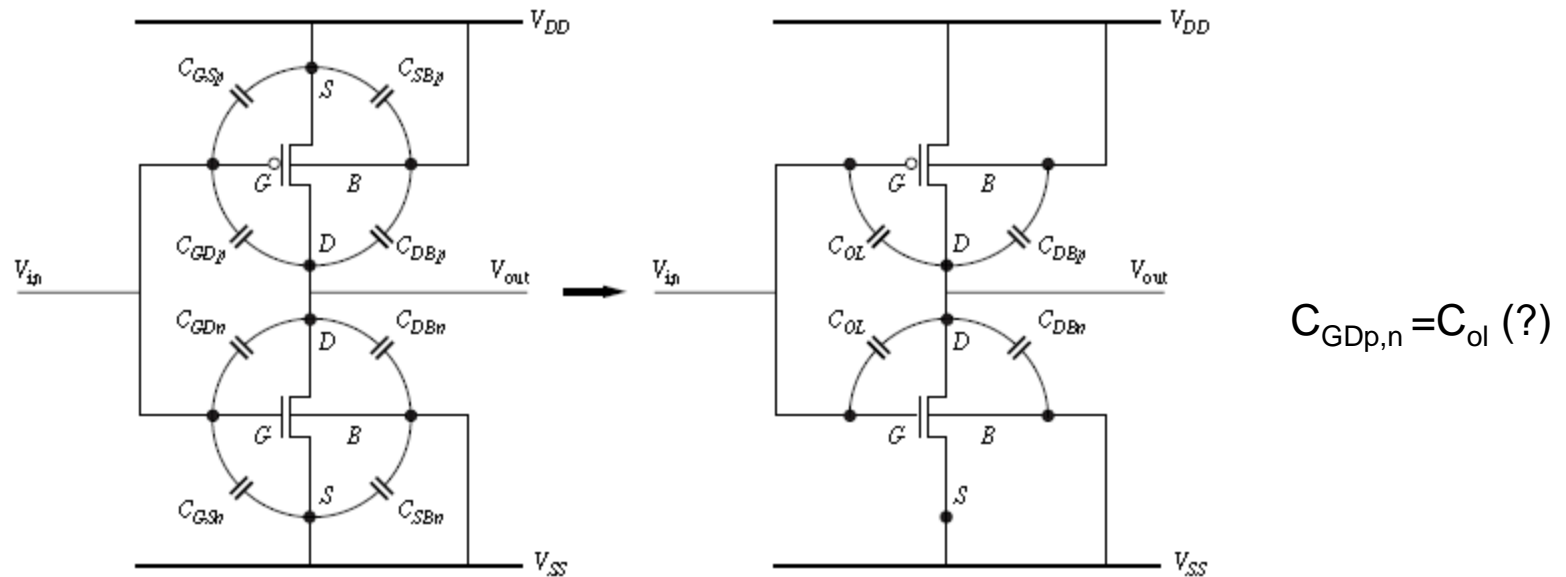

Another term in load calculations is the load presented by

The driver itself (all capacitances connected to  $V_{out}$ )

We have to consider Miller effect! In calculating  $C_{self}$

$$\begin{aligned}
 C_{self} &= C_{DBn} + C_{DBp} + 2C_{OL} + 2C_{OL} \\
 &= C_{jn}W_n + C_{jp}W_p + 2C_{ol}(W_n + W_p) \\
 &= C_{eff}(W_n + W_p)
 \end{aligned}$$




(Board Notes)



# FO1 Inv

   
## FO1 problem

One inverter driving another  
Identical inverter





This picture assumes  $C_g = C_{\text{eff}} = 1 \text{ fF/um}$   
and considers  $C_g * W = C_{\text{eff}} * W = C$


# FO4 & FOM

 

FOM Inverter Loading

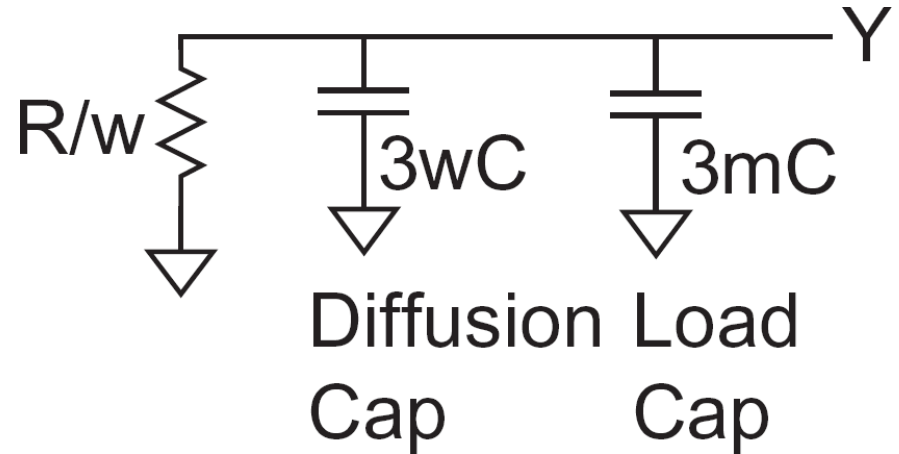 

FOM Loading w/ wider Driver

 

FO4 Inverter Delay ~ 5 - 15ps ( FinFET devices are extremely fast)

# Delay Calculation - Example

---

If a unit transistor has  $R = 10 \text{ k}\Omega$  and  $C = 0.1 \text{ fF}$  in a 65 nm process, compute the delay in the picoseconds of the inverter shown below with a fanout of 4?

