

---

# **ELEC 402**

# **IC Power Consumption**

## **Lecture 15**

Reza Molavi  
Dept. of ECE  
University of British Columbia  
reza@ece.ubc.ca

Slides Courtesy : Prof. Sudip Shekhar (UBC)



# Power & Energy

---

➤ Power is drawn from a voltage source attached to the  $V_{DD}$  pin(s) of a chip.

➤ Instantaneous Power (W):  $P(t) = I(t)V(t)$

➤ Energy (J): 
$$E = \int_0^T P(t)dt$$

➤ Average Power (W): 
$$P_{\text{avg}} = \frac{E}{T} = \frac{1}{T} \int_0^T P(t)dt$$

# Power & Energy in Circuit Elements

$$P_{VDD}(t) = I_{DD}(t)V_{DD}$$




$$P_R(t) = \frac{V_R^2(t)}{R} = I_R^2(t)R$$


 
## Energy Stored in a Capacitor

$$\begin{aligned} E_C &= \int_0^{\infty} I(t)V(t)dt = \int_0^{\infty} C \frac{dV}{dt} V(t)dt \\ &= C \int_0^{V_C} V(t)dV = \frac{1}{2} CV_C^2 \end{aligned}$$



Charging from 0 to  $V_C$

# Charging a Cap through an Inverter

## ➤ When the gate output rises

- Energy stored in capacitor is

$$E_C = \frac{1}{2} C_L V_{DD}^2$$


- But energy drawn from the supply is

$$\begin{aligned} E_{V_{DD}} &= \int_0^{\infty} I(t) V_{DD} dt = \int_0^{\infty} C_L \frac{dV}{dt} V_{DD} dt \\ &= C_L V_{DD} \int_0^{V_{DD}} dV = C_L V_{DD}^2 \end{aligned}$$

- Half the energy from  $V_{DD}$  is dissipated in the PMOS transistor as heat, other half stored in capacitor


 
## ➤ When the gate output falls

- Energy in capacitor is dumped to GND
- Dissipated as heat in the NMOS transistor




# Switching Waveforms

  - Example:  $V_{DD} = 1.0V$ ,  $C_L = 150fF$ ,  $f = 1GHz$



# Switching Waveforms

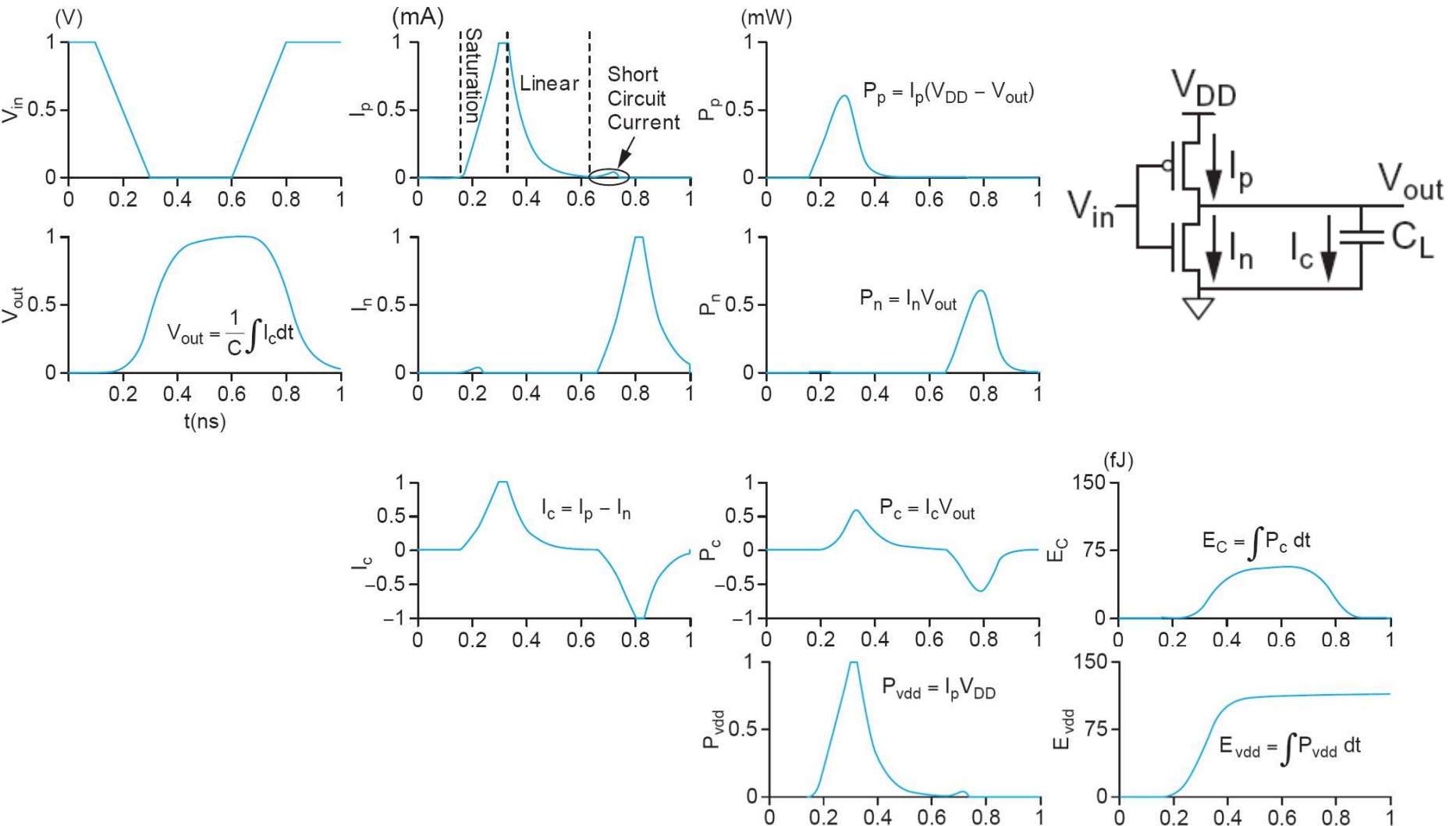- Example:  $V_{DD} = 1.0V$ ,  $C_L = 150fF$ ,  $f = 1GHz$



# Switching Power


$$P_{switching} = \frac{1}{T_{SW}} \int_0^{T_{SW}} i_{DD}(t) V_{DD} dt$$

$$= V_{DD} f_{SW} \int_0^{T_{SW}} i_{DD}(t) dt$$

$$= V_{DD} f_{SW} \int_0^{T_{SW}} C \frac{dv_C}{dt} dt$$

$$= V_{DD} f_{SW} C \int_0^{T_{SW}} \frac{dv_C}{dt} dt = V_{DD} f_{SW} C \int_0^{V_{DD}} dv_C$$

$$= CV_{DD}^2 f_{SW}$$

 

# Activity Factor

---

- Suppose the system clock frequency =  $f$
- Let  $f_{sw} = \alpha f$ , where  $\alpha$  = activity factor = probability that the circuit node transitions from 0 to 1.
  - If the signal is a clock,  $\alpha = 1$
  - If the signal switches once per cycle,  $\alpha = 1/2$
- Dynamic power:

$$P_{\text{switching}} = \alpha C V_{DD}^2 f$$



# Short Circuit Current

---

- When transistors switch, both nMOS and pMOS networks may be momentarily ON at once
- Leads to a blip of “short circuit” current.
- $< 10\%$  of dynamic power if rise/fall times are comparable for input and output
- We will generally ignore this component (as clock period goes further down, i.e. increasing frequency, this assumption becomes less accurate).

# Power Dissipation Sources

---

- $P_{\text{total}} = P_{\text{dynamic}} + P_{\text{static}}$
- **Dynamic power:**  $P_{\text{dynamic}} = P_{\text{switching}} + P_{\text{shortcircuit}}$ 
  - Switching load capacitances
  - Short-circuit current
- **Static power:**  $P_{\text{static}} = (I_{\text{sub}} + I_{\text{gate}} + I_{\text{junct}})V_{\text{DD}}$ 
  - Subthreshold leakage
  - Gate leakage
  - Junction leakage
  - Contention current

# Dynamic Power Example

## ➤ 1 billion transistor chip

- 50M logic transistors
  - Average width:  $12\lambda$
  - Activity factor = 0.1
- 950M memory transistors
  - Average width:  $4\lambda$
  - Activity factor = 0.02
- 1.0V 65nm process ( $\lambda \sim 30$  nm)
- $C = 1$  fF/ $\mu$ m (gate) + 1 fF/ $\mu$ m (diffusion)

## ➤ Estimate dynamic power consumption @ 1 GHz. Neglect wire capacitance (!) and short-circuit current.

$$C_{\text{logic}} = (50 \times 10^6)(12\lambda)(0.030 \mu\text{m} / \lambda)(2 \text{ fF} / \mu\text{m}) = 27 \text{ nF}$$

$$C_{\text{mem}} = (950 \times 10^6)(4\lambda)(0.030 \mu\text{m} / \lambda)(2 \text{ fF} / \mu\text{m}) = 171 \text{ nF}$$

$$P_{\text{dynamic}} = \left[ 0.1 C_{\text{logic}} + 0.02 C_{\text{mem}} \right] (1.0)^2 (1.0 \text{ GHz}) = 6.1 \text{ W}$$

# Dynamic Power Reduction

---

➤  $P_{\text{switching}} = \alpha C V_{DD}^2 f$

➤ **Try to minimize:**

- **Activity factor**
- **Capacitance**
- **Supply voltage**
- **Frequency**

# Activity Factor Estimation

$$P_{\text{switching}} = \alpha C V_{DD}^2 f$$

- Let  $P_i = \text{Prob}(\text{node } i = 1)$ 
  - $\bar{P}_i = 1 - P_i$
- $\alpha_i = \bar{P}_i * P_i$  (node is 0 on one cycle and 1 on the next)
- Completely random data has  $P = 0.5$  and  $\alpha = 0.25$
- Data is often not completely random
  - e.g. upper bits of 64-bit words representing bank account balances are usually 0
- Data propagating through ANDs and ORs have lower activity factor
  - Depends on design, but typically  $\alpha \approx 0.1$

# Switching Probability

$$P_{\text{switching}} = \alpha C V_{DD}^2 f$$

➤ Assuming the inputs are uncorrelated


Gate	$P_Y$
AND2	$P_A P_B$
AND3	$P_A P_B P_C$
OR2	$1 - \bar{P}_A \bar{P}_B$
NAND2	$1 - P_A P_B$
NOR2	$\bar{P}_A \bar{P}_B$
XOR2	$P_A \bar{P}_B + \bar{P}_A P_B$

➤ Activity Factor of the output =  $\bar{P}_Y * P_Y$
 
# Example

$$P_{\text{switching}} = \alpha C V_{DD}^2 f$$


- An AND4 is built out of two levels of gates
- Estimate the activity factor at each node if the inputs have  $P = 0.5$


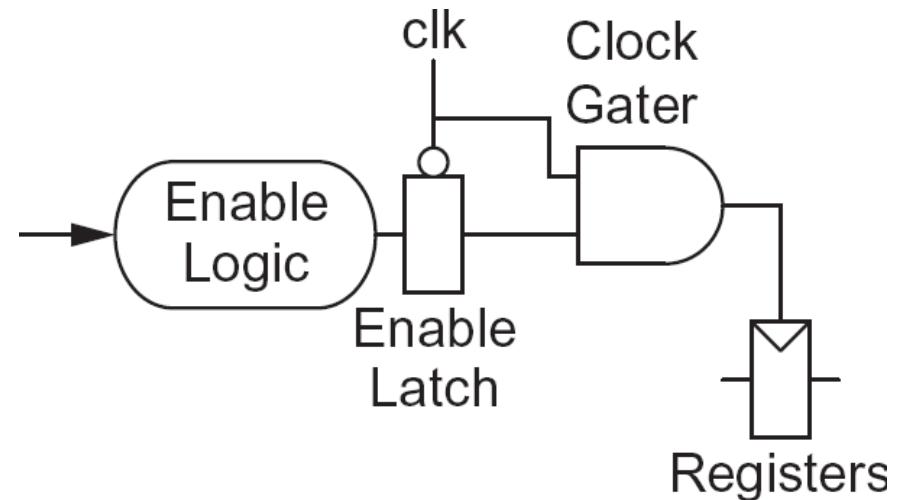
# Clock Gating

$$P_{\text{switching}} = \frac{1}{2} C V_{DD}^2 f$$


- The best way to reduce the activity is to turn off the clock to registers in unused blocks
  - Saves clock activity ( $\alpha = 1$ )
  - Eliminates all switching activity in the block
  - Requires determining if block will be used
  - Disable clock early in the clock distribution network ( $\alpha = 1$ ) and high cap blocks.
  - Use an enable latch to ensure that enable does not change before the clock falls




 
# Capacitance

$$P_{\text{switching}} = \alpha C V_{DD}^2 f$$



## ➤ Gate capacitance

- Fewer stages of logic
- Small gate sizes
- FO8-12 if needed to reduce energy at slight overhead of delay




## ➤ Wire capacitance

- Good floorplanning to keep communicating blocks close to each other
- Drive long wires with inverters or buffers rather than complex gates
   
# Voltage

$$P_{\text{switching}} = \alpha C V^2 f$$

- Run each block at the lowest possible voltage that meets performance requirements
- Voltage Domains
  - Provide separate supplies to different blocks
  - Level converters required when crossing from low to high  $V_{DD}$  domains



# Voltage & Frequency

$$P_{\text{switching}} = \alpha C V^2 f$$

- Run each block at the lowest possible voltage and frequency that meets performance requirements
- Dynamic Voltage Frequency Scaling (DVFS)
  - Adjust  $V_{DD}$  and  $f$  according to workload
  - Cubic reduction in power may be achieved

