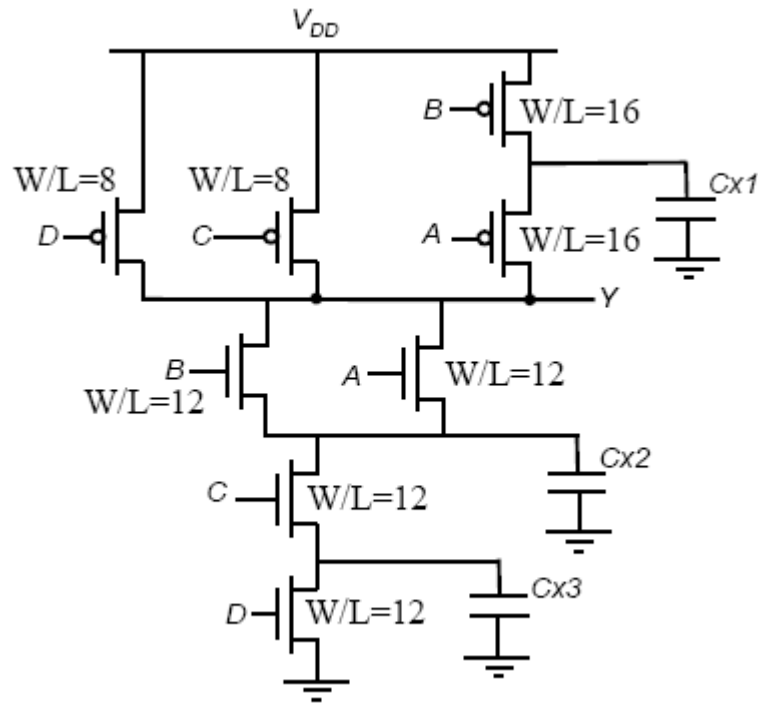


Assignment 4 Analytical Solutions

2)

(a)




(b) Worst case t_{pHL} happens when C_{x2} and C_{x3} have to be discharged. Input pattern before transition should be $ABCD = [1010, 1110, 0110]$ and the final vector should be $ABCD = [1011, 0111]$.

The worst case t_{pLH} happens when C_{x1} has to be charged when the output makes a low to high transition. The input pattern before transition should be $ABCD = [0111]$ and the final vector is $ABCD = [0011]$.

3)

a. $Out = A \cdot sel + B \cdot \overline{sel}$

b.

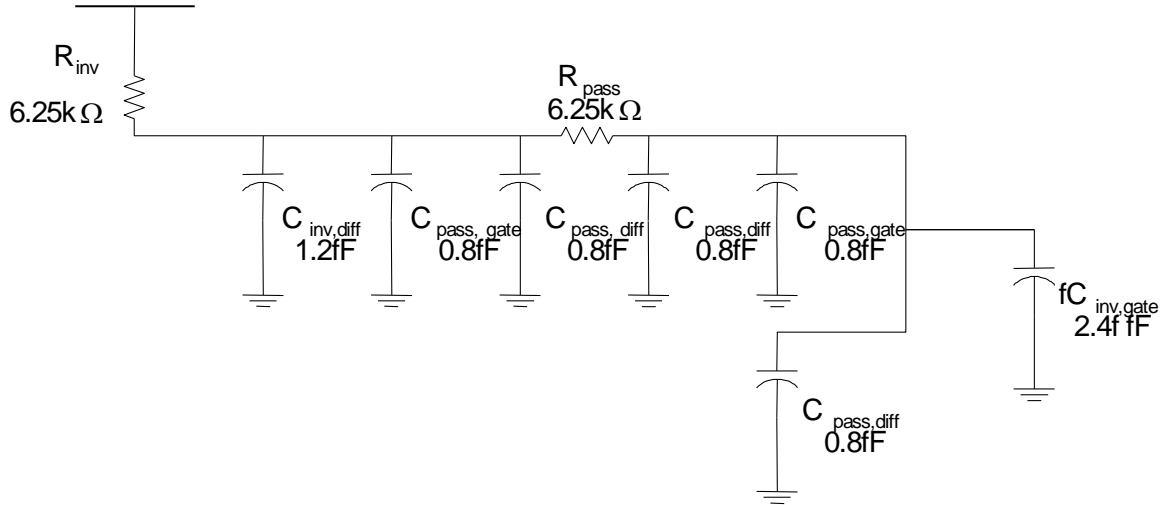

c. $t_{A-C} = R_{inv} (C_{inv,diff} + C_{pass,gate} + C_{pass,diff}) + (R_{inv} + R_{pass}) (fC_{inv,gate} + C_{pass,gate} + 2C_{pass,diff})$

d. $t_{C-out} = \frac{R_{inv}}{f} (fC_{inv,diff} + C_{LOAD}) = R_{inv} C_{inv,diff} + \frac{R_{inv} C_{LOAD}}{f}$

e.

$$t = R_{inv} (C_{inv,diff} + C_{pass,gate} + C_{pass,diff}) + (R_{inv} + R_{pass}) (fC_{inv,gate} + C_{pass,gate} + 2C_{pass,diff}) + R_{inv} C_{inv,diff} + \frac{R_{inv} C_{LOAD}}{f}$$

$$\frac{dt}{df} = (R_{inv} + R_{pass}) (C_{inv,gate}) - \frac{R_{inv} C_{LOAD}}{f^2} = 0$$

$$f = \sqrt{\frac{R_{inv} C_{LOAD}}{(R_{inv} + R_{pass}) (C_{inv,gate})}} = \sqrt{\frac{(6.25k) 50 fF}{(6.25k + 6.25k) (2.4 fF)}}$$

$$= 3.2$$