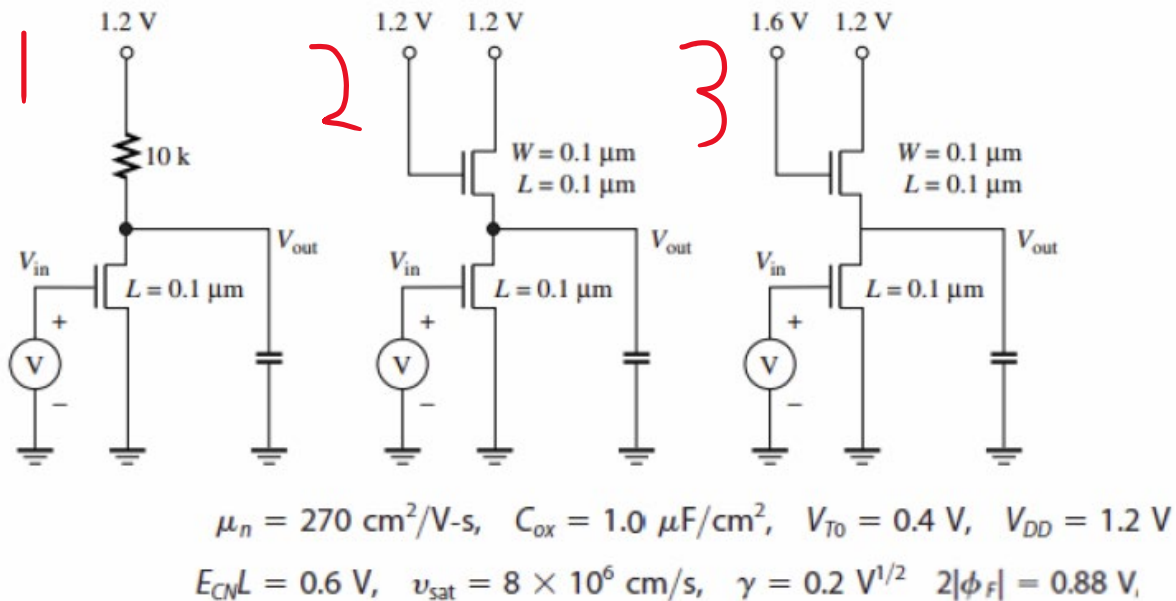


ELEC 402 – October 24, 2021

# Project 3 Report

Martin Chua - 35713411

1. In the circuits of Figure, design the widths of the pull-down transistors so that  $V_{OL} = 0.1$  V. (All transistors are minimum size,  $L = 0.1$   $\mu\text{m}$ .) Explain the results. (15 points)



**a) Resistive load inverter**

At one extreme,  $V_{in}$  is high, transistor is off and no current flows because MOS is in cut-off region,  $V_{OH} = V_{DD}$ . At the other extreme,  $V_{in} = V_{OH} = V_{DD}$  substituted into  $I_{OUT} = I_{load}$  &  $I_R = I_{DS}(\text{lin})$ , and the transistor operates in linear region. Using the useful formula for linear current:

$$\frac{V_{DD} - V_{OL}}{R_L} = \frac{W}{L} * \frac{\mu_n C_{ox}}{1 + \frac{V_{DS}}{E_C L}} \left[ V_{GS} - V_T - \frac{V_{DS}}{2} \right] V_{DS}$$

Now we can also just straight up plug-in everything (taken from question):

- $V_{in} = V_{GS} = V_{OH} = V_{DD} = 1.2 \text{ V}$
- $V_{DS} = V_{out} = V_{OL} = 0.1 \text{ V}$
- $L = 0.1 \text{ } \mu\text{m}$
- $R_L = 10 \text{ k}\Omega$
- $\mu_n = 270 \text{ cm}^2\text{V}^{-1}\text{s}^{-1}$
- $C_{ox} = 1.0\text{E-}6 \text{ F}/\text{cm}^2$
- $E_C = 6 \text{ V}/\mu\text{m}$
- $V_T = 0.4 \text{ V}$

Equating for  $W$  and throwing into wolfram:

$$W = 6.3375 * 10^{-7} \text{ m} = 0.634 \text{ } \mu\text{m}$$

**b) Saturated-enhancement-load inverter**

With this layout, we know the top pull-up transistor is the load and bottom pull-down transistor is the inverter. We know the load is always in saturation and the inverter should be linear because we want

$V_{out} = V_{OL} = 0.1$  V. Using the useful formulas for linear (left) and saturated (right) current, we can equate the two and get:

$$\frac{W_{inverter}}{L} * \frac{\mu_n C_{ox}}{1 + \frac{V_{DS}}{E_C L}} \left[ V_{GS} - V_T - \frac{V_{DS}}{2} \right] V_{DS} = W_{load} v_{sat} C_{ox} * \frac{(V_{GS} - V_T)^2}{V_{GS} - V_T + E_C L}$$

Using the following substitutions (inverter):

- $V_{in} = V_{GS} = V_{OH} = V_{DD} = 1.2$  V
- $V_{DS} = V_{out} = V_{OL} = 0.1$  V
- $L = 0.1$   $\mu$ m
- $\mu_n = 270$   $\text{cm}^2\text{V}^{-1}\text{s}^{-1}$
- $C_{ox} = 1.0\text{E-}6$  F/ $\text{cm}^2$
- $E_C = 6$  V/ $\mu$ m
- $V_T = 0.4$  V

Using the following substitutions (load):

- $V_{in} = V_{OH} = V_{DD} = 1.2$  V
- $V_{GS} = 1.2 - 0.1 = 1.1$  V
- $v_{sat} = 8\text{E}6$  cm/s
- $W_{load} = 0.1$   $\mu$ m
- $L = 0.1$   $\mu$ m
- $C_{ox} = 1.0\text{E-}6$  F/ $\text{cm}^2$
- $E_C = 6$  V/ $\mu$ m
- $V_T = 0.4$  V

Note that although the left side units cancel out nicely due to the  $\text{cm}^2/\text{cm}^2$ , we need to convert the right-side units from cm (1E-2) to  $\mu$ m (1E-6) after the  $C_{ox}v_{sat}$  cancellation as there is still a cm unit left, done by multiplying the right side with 1E-4.

Equating for  $W_{inverter}$  and throwing into wolfram:

$$W_{inverter} = 1.73726 * 10^{-7} \text{ m} = 0.174 \text{ } \mu\text{m}$$

### c) Linear-Enhancement-Load inverter

To overcome low  $V_{OH}$ , in the saturated-enhancement-load inverter, instead of  $V_{DD}$  for both gate and drain of the load transistor, it is separated with  $V_{GG} = 1.6$  V and  $V_{DD} = 1.2$  V. Its linear region of operation is then  $V_{GG} > V_{DD} + V_{TL}(V_{DD})$ . Again, we equate currents but this time, the right side is not in saturation, but linear operation as well:

$$\frac{W_{inverter}}{L} * \frac{\mu_n C_{ox}}{1 + \frac{V_{DS}}{E_C L}} \left[ V_{GS} - V_T - \frac{V_{DS}}{2} \right] V_{DS} = \frac{W_{load}}{L} * \frac{\mu_n C_{ox}}{1 + \frac{V_{DS}}{E_C L}} \left[ V_{GS} - V_T - \frac{V_{DS}}{2} \right] V_{DS}$$

Using the following substitutions (inverter):

- $V_{in} = V_{GS} = V_{OH} = V_{DD} = 1.2$  V
- $V_{DS} = V_{out} = V_{OL} = 0.1$  V
- $L = 0.1$   $\mu$ m
- $\mu_n = 270$   $\text{cm}^2\text{V}^{-1}\text{s}^{-1}$
- $C_{ox} = 1.0\text{E-}6$  F/ $\text{cm}^2$
- $E_C = 6$  V/ $\mu$ m
- $V_T = 0.4$  V

Using the following substitutions (load):

- $V_{in} = V_{DS} = V_{OH} = V_{DD} = 1.2$  V
- $V_{out} = V_{OL} = 0.1$  V
- $V_{GS} = 1.6 - 0.1 = 1.5$  V
- $L = 0.1$   $\mu$ m
- $\mu_n = 270$   $\text{cm}^2\text{V}^{-1}\text{s}^{-1}$
- $C_{ox} = 1.0\text{E-}6$  F/ $\text{cm}^2$
- $E_C = 6$  V/ $\mu$ m
- $V_T = 0.4$  V

Note that the difference this time between linear-enhancement and saturated-enhancement is  $V_{GS}$  of the load pull-up transistor. Also note that  $V_{in}$  for the linear region inverter pull-down transistor remains at 1.2 V.

Equating for  $W_{inverter}$  and throwing into wolfram (no need to simplify if wolfram does it all 😊):

$$W_{inverter} = 1.4 * 10^{-7} m = 0.140 \mu m$$


#### d) Results explanation

Resistive Load	Saturated-Enhancement-Load	Linear-Enhancement-Load
0.634 $\mu m$	0.174 $\mu m$	0.140 $\mu m$

Table 0. Calculated widths for each inverter.

The resistive load inverter appears to have the highest width, followed by Saturated-Enhancement, then Linear-Enhancement. The resistor in digital design is probably worse than using a MOSFET due to area which in turn means a slower and larger circuit. The Saturated-Enhancement load inverter replaces the resistor with a MOSFET, where the max input voltage is limited by  $V_{DD} - V_{T,}$ , which has tradeoffs such a lower saturation operation threshold. The Linear-Enhancement load inverter introduces a higher  $V_{GG}$ , which means that biasing the gate voltage to exactly  $V_T$  above drain voltage allows linear operation and increases the saturation operation threshold.

 2. (a) What is the intended function of the circuit shown in Figure ?  
What is the output swing?



- (b) Draw the dc voltage transfer characteristic of the above gate. Label  $V_{OL}$  and  $V_{OH}$ , and any other interesting values in the VTC. Since the gate has hysteresis, be sure to handle both the rising and falling cases.
- (c) What is the gain of the circuit? Is this a valid gate (i.e., does it have the needed noise rejection properties)?
- (d) Use CAD to validate your solution by plotting the VTC (20 points)

- For CAD simulation in Q2 assume  $V_{DD} = 0.9$  V, and use two fingers per transistor.

- a) The intended function of the circuit should be as a non-inverting buffer. It resembles an inverter except the PMOS and NMOS are switched, with the  $V_{out}$  at the source. If we set logic in to be HIGH, we get HIGH as output, and vice-versa setting logic in to LOW, gets LOW as output, with

$V_{OH}$  being maximum  $V_{DD} - V_T$  due to NMOS pull-up and  $V_{OL}$  being minimum  $V_T$  due to PMOS pull-down, assuming same threshold voltage  $V_T$  for both PMOS and NMOS.

- b) The dc voltage transfer characteristic is drawn below with the following notes:
- We start from  $V_{in} = 0$  V and output is  $V_{OL} = V_T$  and increase the voltage. The output should not change until NMOS turns on and pulls output up at  $V_{in} = 2V_T$ .
  - Output voltage increases as input voltage increases until  $V_{DD}$ , where output is at most  $V_{OH} = V_{DD} - V_T$ .
  - When decreasing  $V_{in}$ , the output does not decrease until  $V_{in}$  drops below  $V_{DD} - V_T$ .
  - Then at  $V_{DD} - 2V_T$  we see that the output decreases until  $V_T$  is reached at output, or  $V_{OL}$

 


Figure 1. DC Voltage Characteristic of a 'Non-inverting Buffer' depicting hysteresis

- c) Ideally, gain should be 1. However from the plot, we see slopes that indicate not 1, because of the fact that  $V_{in}$  of 0 to  $V_{DD}$  does not correspond to a  $V_{in}$  of 0 to  $V_{DD}$ , but rather  $V_{OL}$  to  $V_{OH}$  which each differ by  $V_T$ . Also, the output high and low must be above and below  $V_{IL}$  respectively, which is not the case. Thus the circuit is not a valid gate. Output is not ideal; output low is not tied to zero, but rather  $V_T$  because the PMOS turns off before  $V_{OL}$  reaches 0 V.
- d) CAD Tool Validation with  $V_{DD} = 0.9$  V. Here is the buffer:

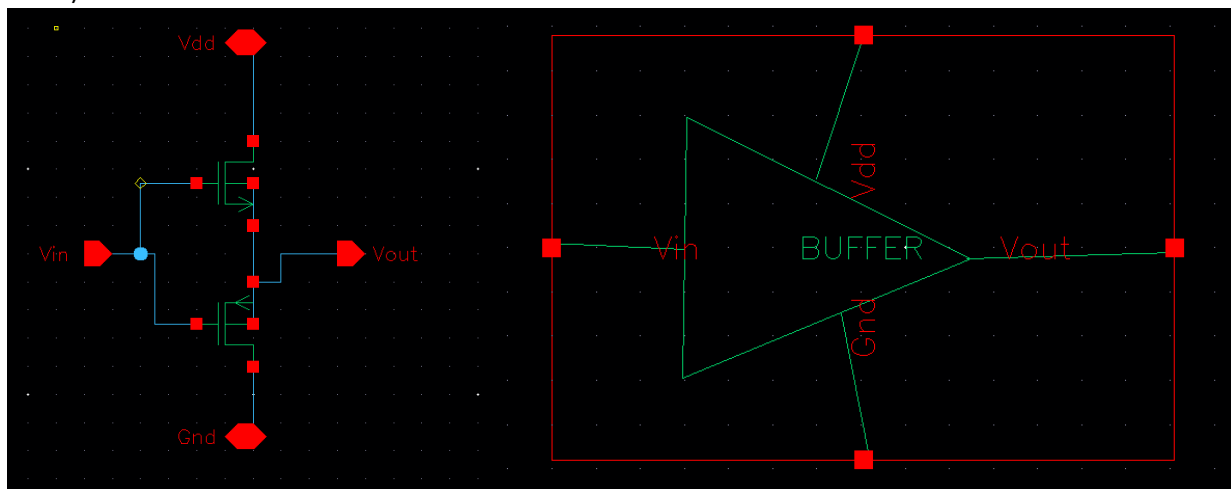


Figure 2. Buffer schematic (left) and buffer symbol (right)

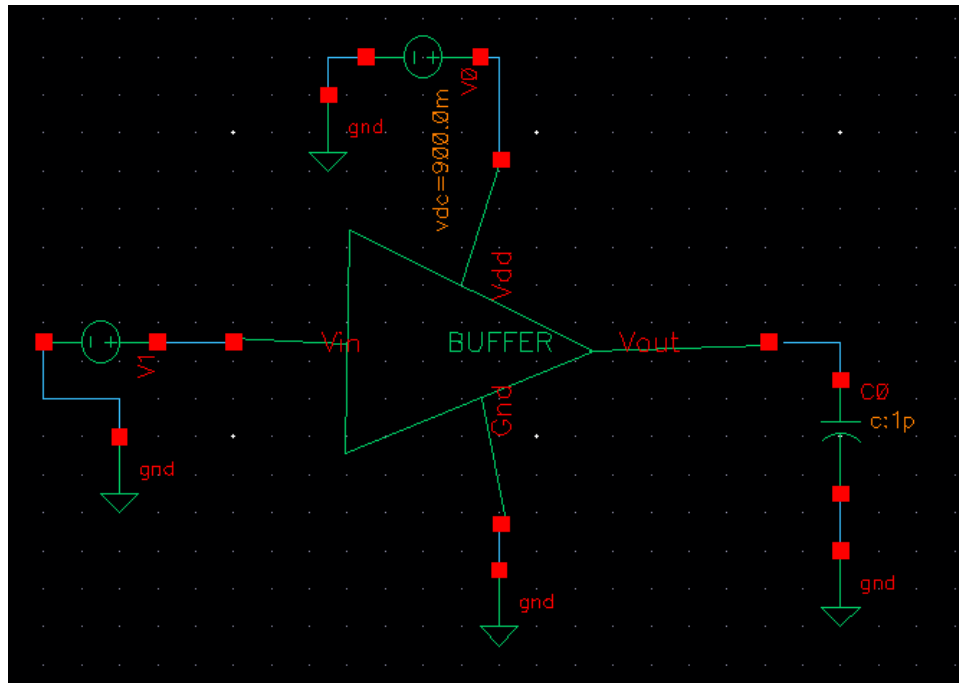


Figure 3. Buffer test bench circuit with  $V_{dd} = 0.9\text{ V}$  and  $V_{out}$  attached to 1pF capacitor.



Figure 4. Sweep of  $V_{in}$  from 0 to 0.9 V (Green) with output  $V_{out}$  (Red).



Figure 5. Differences in Input vs Output (Not exactly 0 to  $V_{DD}$ )


 


Figure 6. Derivative of output.

From figure 5, we can see that there are differences between  $V_{in}$  and  $V_{out}$  and it does not match 1:1 due to the bound of  $V_T$ . Figure 6 tells us information about the gain. Although it has a high gain region between two low gain regions, the gain must be greater than 1 for the high gain region, so the design is still invalid. Hysteresis is difficult to see in the outputs, which can be explained that perhaps there is not much hysteresis as is exaggerated by the hand-drawn plot in figure 1.

 3. Figure shows a circuit used to measure the effective value of body effect factor ( $\gamma$ ) (by measuring  $V_T$  at different source voltages) and channel length modulation factor ( $\lambda$ ) (by measuring  $I_d$  at different  $V_{ds}$  values). Assume in formula for threshold voltage (slide 7 lecture set 4 – MOS basics),  $2\phi_F = 0.88$  V, and calculate  $V_{T0}$ ,  $\gamma$ , and  $\lambda$  for a device with 2 fingers. Can you justify the value of  $\gamma$  for the FinFET device you are simulating? Attach your CAD netlist, graphs and measurement data to your answers **(25 points)**



a) Body effect factor

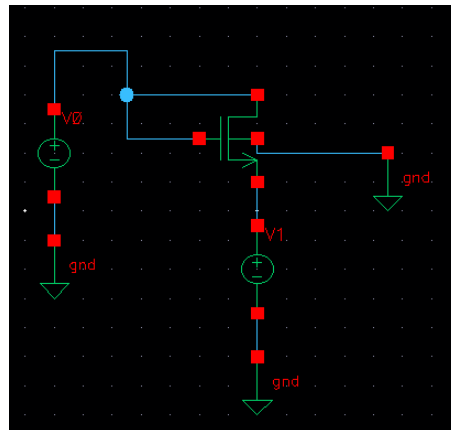


Figure 7. Body Effect schematic

We measure  $V_T$  at different source voltages.  $V_2$  is fixed to a certain value, and DC sweep is performed for  $V_1$  from 0 to 5 V and  $V_T$  is measured at the point where current rises, with arbitrary threshold at  $1 \mu\text{A}$ .



 


Figure 8. Sample plot of  $V_{in}$  vs  $I_{DS}$ , where marker is placed at threshold of  $1 \mu A$ .  $V_T$  is recorded and put into a table. Note that for all  $V_2 > 0$ , we will need to subtract  $V_T$  by  $V_2$  since that  $V_{DS} = V_1 - V_2$ .

$V_2$ (V)	$V_{raw}$ (V)	$V_T$ (V)
0	1.653	1.653
0.1	1.752	1.652
0.2	1.850	1.650
0.3	1.949	1.649
0.4	2.048	1.648
0.8	2.443	1.643
1.1	2.740	1.640
1.5	3.137	1.637

Table 1. Values collected for  $V_T$  while varying  $V_2$ .

Now we can use the formula below to calculate body-effect:

$$V_T = V_{T_0} + \gamma (\sqrt{V_{SB} + |2\phi_f|} - \sqrt{|2\phi_f|})$$

We're given  $2\phi_f$  in the question, and  $V_{T_0}$  is calculated to be 1.653 when  $V_{SB} = 0$ .  $V_{SB}$  is  $V_2$ .

$V_2$ (V)	$V_T$ (V)	$\gamma (\sqrt{V})$
0	1.653	0
0.1	1.652	-0.01928
0.2	1.650	-0.02966
0.3	1.649	-0.02699
0.4	1.648	-0.02587
0.8	1.643	-0.02793
1.1	1.640	-0.02772

1.5	1.637	-0.02646
-----	-------	----------

Table 2. Calculated body-effect using formula above

$$=(H6-1.653)/(SQRT(G6+ABS(0.88))-SQRT(ABS(0.88)))$$

D	E	F	G	H	I
			V	VT	gamma
			0	1.653	#DIV/0!
			0.1	1.652	-0.01928
			0.2	1.65	-0.02966
			0.3	1.649	-0.02699
			0.4	1.648	-0.02587
			0.8	1.643	-0.02793
			1.1	1.64	-0.02772
			1.5	1.637	-0.02646

Figure 9. Excel calculated value with formula at top of figure.

Thus we see that body-effect varies from  $\sim -0.02$  to  $-0.026$  given varying voltage between source and substrate bulk. Since  $V_T$  is basically constant for varying levels of  $V_{GS}$ , we can conclude that body effect has a minimal effect on the threshold voltage of the transistor and is relatively insignificant in this case.

Netlist is below:

```

** Generated for: hspiceD
** Generated on: Oct 25 22:40:24 2021
** Design library name: ELEC402
** Design cell name: blackbody
** Design view name: schematic
.PARAM v1=1 v0=0

.PROBE DC
+ I2(m0)
.DC v0 0.0 5.0 1e-3

.TEMP 25.0
.OPTION
+ ARTIST=2
+ INGOLD=2
+ PARHIER=LOCAL
+ PSF=2
.LIB "/ubc/ece/data/cmc2/kits/ncsu_pdk/FreePDK15/hspice/models/fet.inc" CMG

** Library name: ELEC402
** Cell name: blackbody
** View name: schematic
m0 net1 net1 net2 0 nfet AD=608e-18 AS=608e-18 PD=168e-9 PS=168e-9 M=2
v1 net2 0 DC=1.5
v0 net1 0
.END

```

Figure 10. Netlist for Q3 circuit.

b) Channel Length modulation factor ( $\lambda$ )



Figure 11. Setting sweep of  $V_{DS}$  from 0 to 100 V.

Below two methods will be used: method one uses figure 11 with a very high  $V$  (also rip transistor). Method two sweeps to 5 V and draws a line yielding a similar result for channel length modulation factor (intercept at  $\sim 4.6V - 1.65 = 2.95V = V_{GS}$ ). See figure 12.

 


Figure 12. Sweep from 0 to 5 volts. This yields a similar result to finding the derivative for the hyperbole sweep if a best-fit line is drawn to find the intercept.

# Channel-length Modulation ( $I_{DS}$ dependence on $V_{DS}$ )

$$I_{DS} = \frac{k}{2} (V_{GS} - V_T)^2 (1 + \lambda V_{DS})$$

Large drain-source voltage makes the channel effectively smaller, i.e. larger drain current

The reduction in the effective length is due to the increase in the depletion width of reverse-biased junction.

 


Figure 13. Slide on how to find channel length modulation.

 


Figure 14. Derivative to get slope of linear  $\approx 2.77211E33$ .



Knowing a point (23.1253, 55.6863E33) we can use  $y = mx + b$ , and solve for  $b$  first, then get point at which  $y = 0$ :


$$\begin{aligned}y &= mx + b \\55.6863E33 &= 2.77211E33(23.1253) + b \\b &= -8.4196E33\end{aligned}$$

For  $(x, 0)$ :

$$\begin{aligned}y &= 2.77211E33(x) - 8.4196E33 \\0 &= 2.77211E33(x) - 8.4196E33 \\x &= 3.03725\end{aligned}$$

This is similar to the intercept we get with a 0-5V sweep, 2.95 V. See text above figure 12 for context. Following figure 13, we get  $\lambda = 1/x \approx 0.329$  or  $0.339$  depending on following the 100 V sweep or 5 V sweep.

 4. Consider the layout in the figure below implemented in a 180nm technology. Assume that the transistor has  $W=900\text{nm}$ ,  $L=180\text{nm}$  and a source/drain dimension  $Y=800\text{nm}$  and a lateral diffusion of  $22\text{nm}$ . Let  $t_{ox}=40\text{ \AA}$  (Angstroms). ( 12 points)



- Compute the worst case gate capacitance per unit width,  $C_g$ , in units of  $\text{fF}/\mu\text{m}$ . Estimate  $C_{gs}$ ,  $C_{gd}$  and  $C_{gb}$  in linear, saturation and cutoff, including overlap effects.
- If  $N_A=3 \times 10^{16}/\text{cm}^3$  and  $N_D=3 \times 10^{19}/\text{cm}^3$ ,  $x_j=300\text{nm}$ , compute the worst-case capacitance value per unit width,  $C_j$ , in units of  $\text{fF}/\mu\text{m}$ .
- Compute the drain junction capacitance for the following cases ( $m=0.5$ ):
  - $V_D=1.8\text{V}$ ,  $V_B=0\text{V}$
  - $V_D=0\text{V}$ ,  $V_B=0\text{V}$

a) First we need  $C_{ox}$ , computed using:

$$C_{ox} = \frac{\epsilon_{ox}}{t_{ox}} = \frac{3.9\epsilon_0}{40E-10} = 8.63283E-3 \frac{F}{m^2}$$

$\epsilon_{ox}$  is the  $\text{SiO}_2$  permittivity \* free space permissibility (F/m). Thickness (m),  $t_{ox}$ , is given in the question.

We also need  $C_{ov}$  computed using:

$$C_{ov} = C_{ox} * L_{diffusion} = 1.8992226E - 10 \frac{F}{m}$$

$L_{diffusion}$  is given in the question (m), and we've just previously solved for  $C_{ox}$ , (F/m<sup>2</sup>). We can also assume fringe capacitance  $C_f$  is 0 since  $T_{poly}$  is not given.

We also need worst total gate capacitance  $C_g$  per unit width:

$$C_g = C_{ox}L = 1.5539094E - 9 \frac{F}{m} = 1.554 \frac{fF}{\mu m}$$

$L$  is given in question (m). Overlap is not included.

If we include overlap, then it becomes:

$$C_{go} = 2C_{ov} + C_g = 1.93375392E - 9 \frac{F}{m} = 1.93 \frac{fF}{\mu m}$$

There is two of  $C_{ov}$  due to parallel capacitances. Width isn't in calculation because this is in terms of unit width.

	Cutoff	Linear	Saturation
$C_{GS}$	$C_{ov}$	$1/2C_gW + C_{ov}$	$2/3C_gW + C_{ov}$
$C_{GD}$	$C_{ov}$	$1/2C_gW + C_{ov}$	$C_{ov}$
$C_{GB}$	$C_gW$	0	0

Table 3a. Capacitance equations for gate-source, gate-drain, gate-bulk.

	Cutoff	Linear	Saturation
$C_{GS}$	0.19	0.89	1.12
$C_{GD}$	0.19	0.89	0.19
$C_{GB}$	1.4	0	0

Table 3b. Capacitance values for gate-source, gate-drain, gate-bulk. Units in fF/ $\mu m$

b) Now we want to find  $C_j$  in units of fF/ $\mu m$ . We first need the voltage asymptote  $\phi_B$ :

$$\phi_B = \frac{kT}{q} \ln \left( \frac{N_A N_D}{n_i^2} \right) = 0.936 V$$

These constants are from the question.

Now we want  $C_{jb}$ :

$$C_{jb} = \sqrt{\frac{\epsilon_{Si} q N_A N_D}{2 \phi_B n_i^2}} = 0.516 \frac{fF}{\mu m^2}$$

We use Si permittivity \* free space permissibility.

Now we can solve for  $C_j$ :

$$C_j = \frac{C_{jb}(Y + 2x_j)W}{\left(1 - \frac{V_j}{\phi_B}\right)^m} = C_{jb}(Y + 2x_j)W = 0.650 fF$$

$M$  is 0.5. Worst case takes into account both sides as well as  $V_j = 0 V$ .  $Y$  is given in the question, and so is  $x_j$  and  $W$ .

c) Drain junction capacitance equation is the same as in b, but just single  $x_j$ :

$$C_{drain} = \frac{C_{jb}(Y + x_j)W}{\left(1 - \frac{V_j}{\phi_B}\right)^m}$$

- i. With  $V_j = -1.8$  V, we get  $C_j = 0.299$  fF.
- ii. With  $V_j = 0$  V, we get  $C_j = 0.511$  fF.

5. A CMOS inverter in 45 nm technology has a pull-up device that is  $8\lambda:2\lambda$  and a pull-down device that is  $4\lambda:2\lambda$ . It drives four identical inverters at its output. Compute the inverter delay (use  $C_g = 2$  fF/ $\mu m$ ) and assume a ramp input. Re-calculate the delay if we have a chain of 4 inverters, i.e. 4 inverters in series **(13 pts)** Note:  $2\lambda = 45$ nm

- a) Inverter delay with four identical inverters at output. Pull-up means PMOS W/L  $8\lambda:2\lambda$ , pull-down means NMOS W/L  $4\lambda:2\lambda$ . Assuming  $C_g = 1$ fF/ $\mu m$  from the useful formulas, knowing that  $2\lambda = 45$ nm:

$$C_L = C_g * (W_n + W_p) = \frac{2fF}{\mu m} * (4 * 0.09\mu m + 4 * 0.18\mu m) = 2.16 fF$$

The 4 times is for the parallel capacitances at the output of the inverter. Similarly:

$$C_{self} = C_{eff} * (0.09\mu m + 0.18\mu m) = 0.27 fF$$

And then we can sum the two to get the total capacitance:

$$C_{total} = C_{self} + C_L = 2.43 fF$$

For delay, as given in class we can approximate the resistance as  $R = R_{eqn} (L/W)$ , where 45nm  $R_n$  is  $34k \Omega \mu m$  and  $R_p$  is  $68 k\Omega \mu m$ . We also know that ramp is just RC:

$$\tau_{ramp}^n = \tau_{ramp}^p = RC = 34 k\Omega * \frac{1}{2} * C_{total} = 41.31 ps$$

- b) Inverter delay with series of 4 identical inverters, so 5 inverters in total in series.

Each inverter would have an equivalent  $C_{self} = 0.27$  fF. Since its cascading, we can simply multiply by 5 to get the equivalent  $C_{total} = 5C_{self} = 1.35$  fF. The load here is a wire. Thus:

$$\tau_{ramp}^n = \tau_{ramp}^p = RC = 34 k\Omega * \frac{1}{2} * C_{total} = 22.95 ps$$

## References:

Useful physical constants: <https://onlinelibrary.wiley.com/doi/pdf/10.1002/9781119009597.app3>