

---

# ELEC 402

## Dynamic Logic Design (Domino Logic) Lecture 13


Reza Molavi  
Dept. of ECE  
University of British Columbia  
reza@ece.ubc.ca

Slides Courtesy : Dr. H. Djahanshahi (Microsemi), and Dr. Res Saleh (UBC)

---

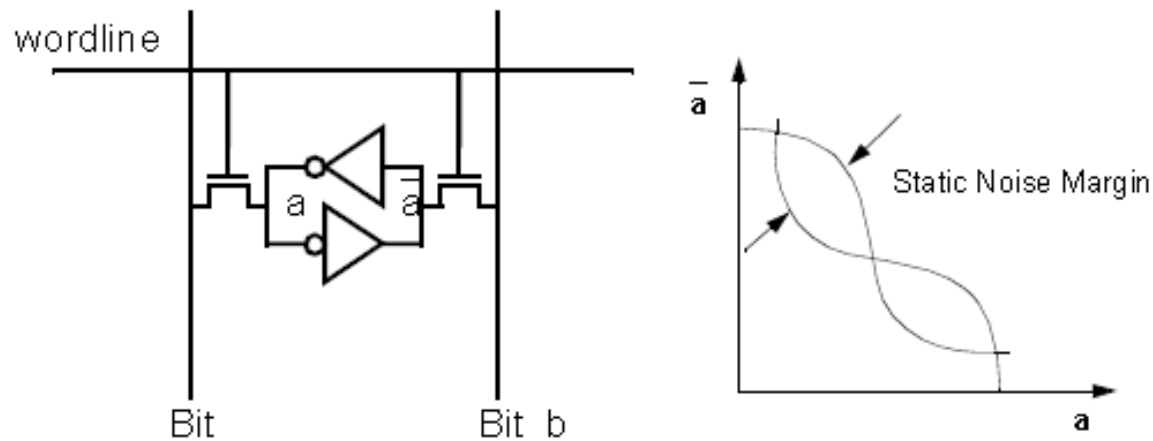
# Building a Storage Cell – SRAM Basic

Uses only six transistors (called 6T cell):




Read and write operations use the same port. There is one wordline and two bit lines. The bit lines carry complementary data. The cell layout is small since it has a small number of wires.

# Dynamic Latch

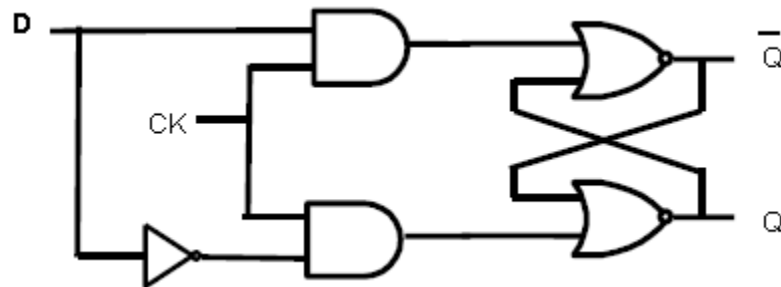


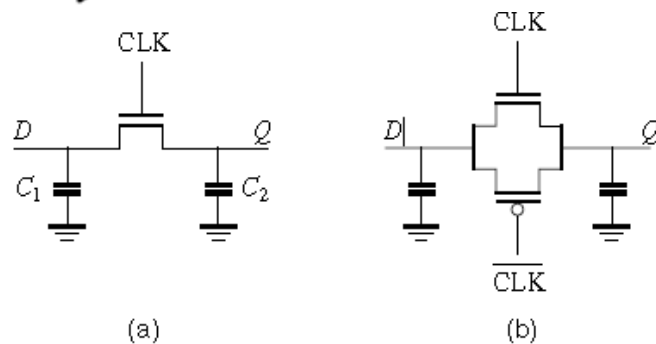Remember D-latch from previous chapters  
(main building block of sequential logic)




All three do D-latch, however they have several  
Issues:

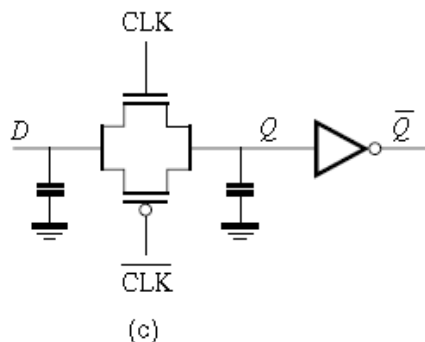
- a) For  $D=1$ , output only reaches  $V_{DD} - V_T$ 
  - Clock feedthrough
- a) No complementary output!
- b) still prone to all dynamic logic problems  
(leakage, cross-talk, etc)
  - When  $clk$  is low, what can we do?



# Dynamic Latch - II

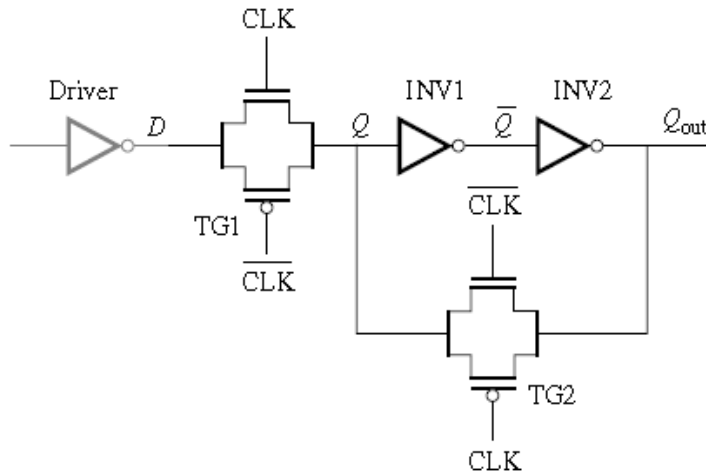


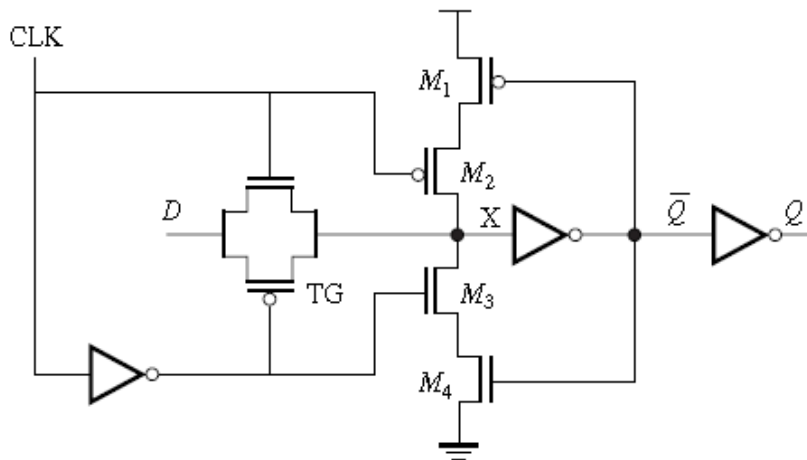The feedback path ensures that the Value of  $Q$  is maintained while  $CLK = 0$  (the feedback  $TG2$  should be weak to avoid Conflict)



Another popular structure of D-latch  
(note that if  $X=Q=1$ , the pull-up path creates a Feedback and holds the value and if  $X=Q=0$ , the Pull-down path is responsible for the feedback)


# Dynamic D FF (Master-Slave)

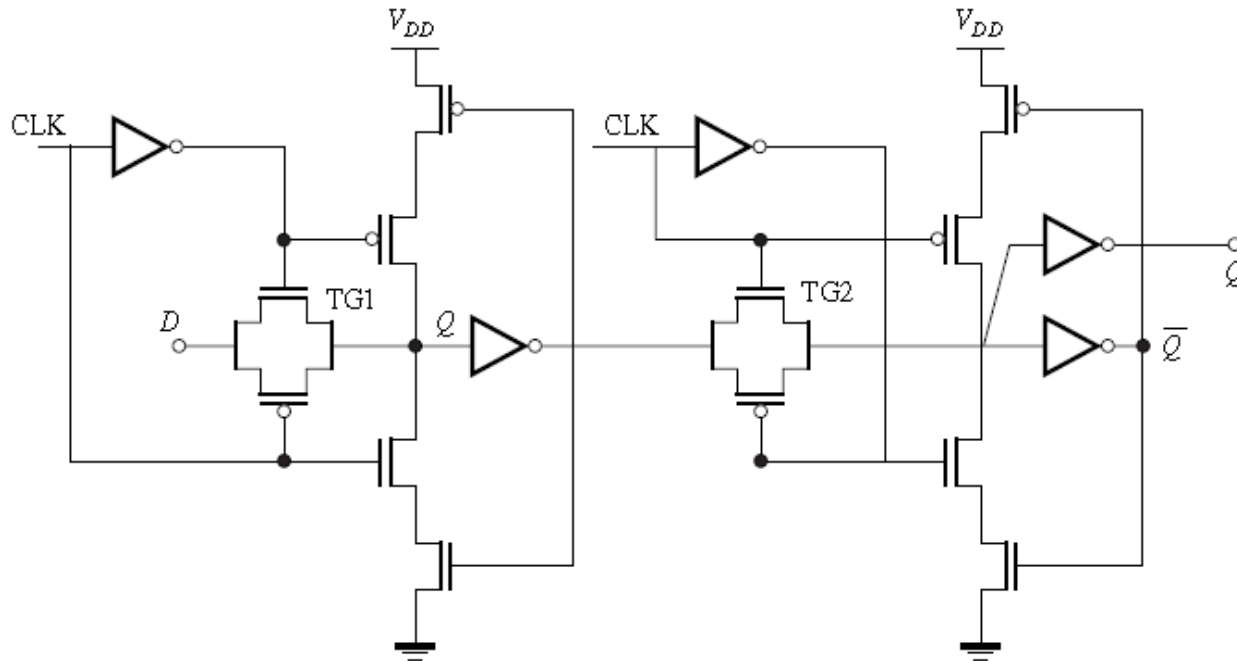

“Positive edge-triggered Master-Slave D Flip-flop”

When the clock goes high, the Master latch shuts-off and holds its value at internal  $Q$  while the slave latch becomes transparent and passes the  $Q$  to the output, the overall action is sampling  $D$  at this moment (rising edge of  $CLK$ )

# Dynamic Logic vs. Static Logic

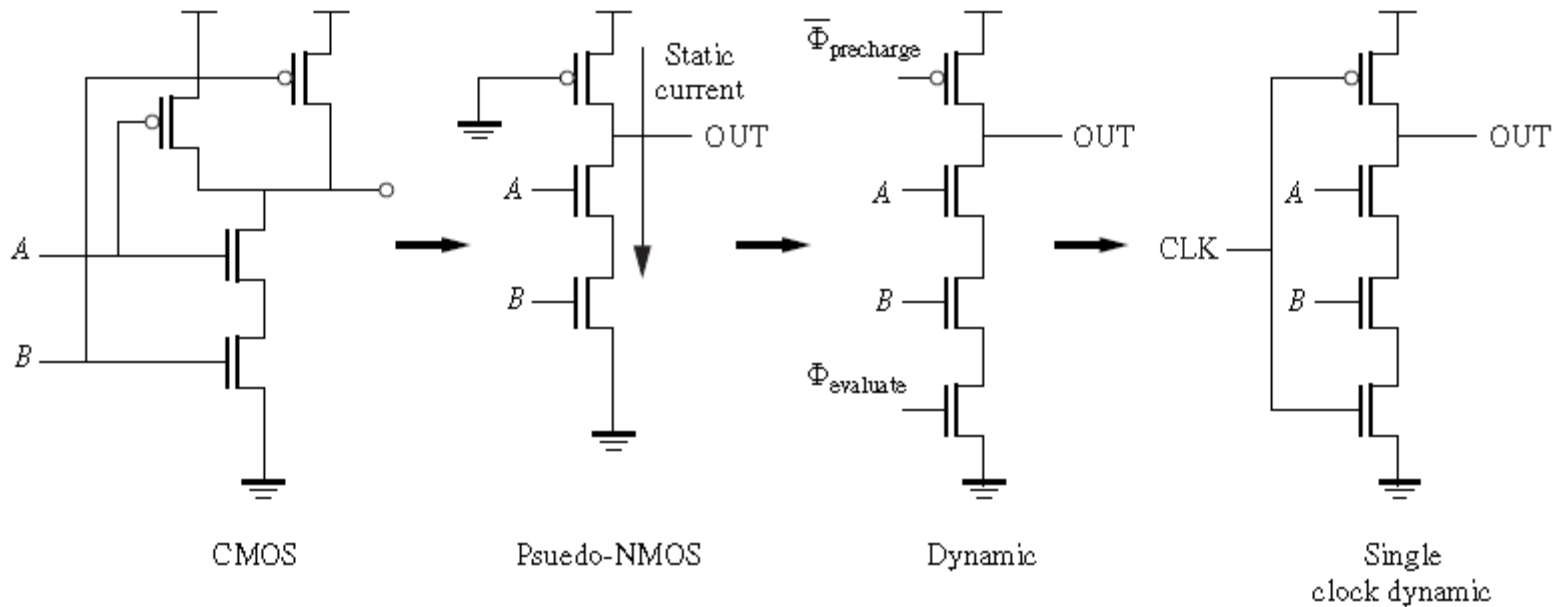

Pseudo NMOS has only one pull-up device but consumes static power, why not turn it off then?

Dynamic logic uses similar structure to pseudo-NMOS (an extra foot NMOS), using a CLK

During the **pre-charge** phase, PMOS pulls-up the OUT, during **evaluation** phase the pull-down


Network gets activated and decides whether to discharge OUT (or not).

## Design using Dynamic Logic - Example


---

Implement a 3-input NOR gate in dynamic logic and explain its operation. Size the transistors to deliver the same delays as a conventional CMOS inverter (PMOS  $8\lambda:2\lambda$ , NMOS  $4\lambda:2\lambda$ ).

# Domino Logic

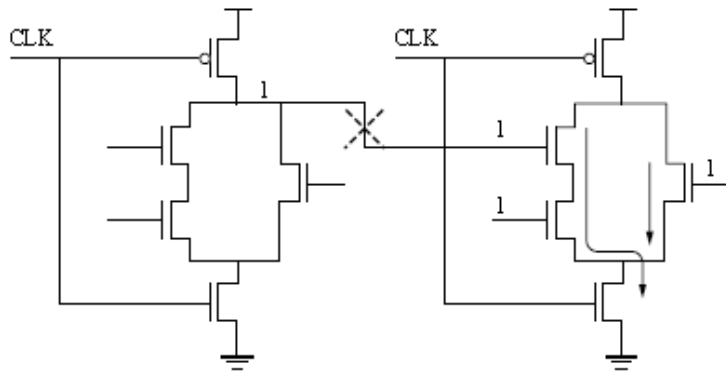

(a) Direct connection not possible

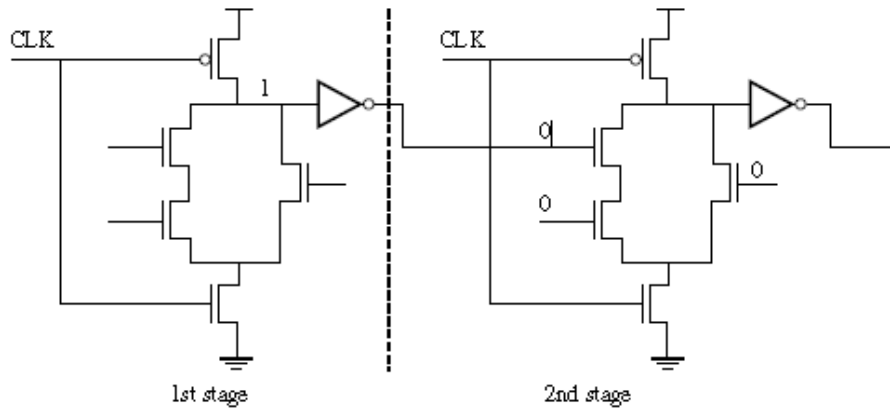

(b) Insert inverter between dynamic gates


In dynamic logic every output node is pre-charged to  $V_{dd}$ , therefore, a direct connection between cascaded stages causes malfunction (during the evaluation it always goes low)

To avoid the issue we define the logic as dynamic logic+inverter, therefore after Precharge all inputs are low, this is called Domino logic

- Only for non-inverting functions



# Cascaded Domino Logics

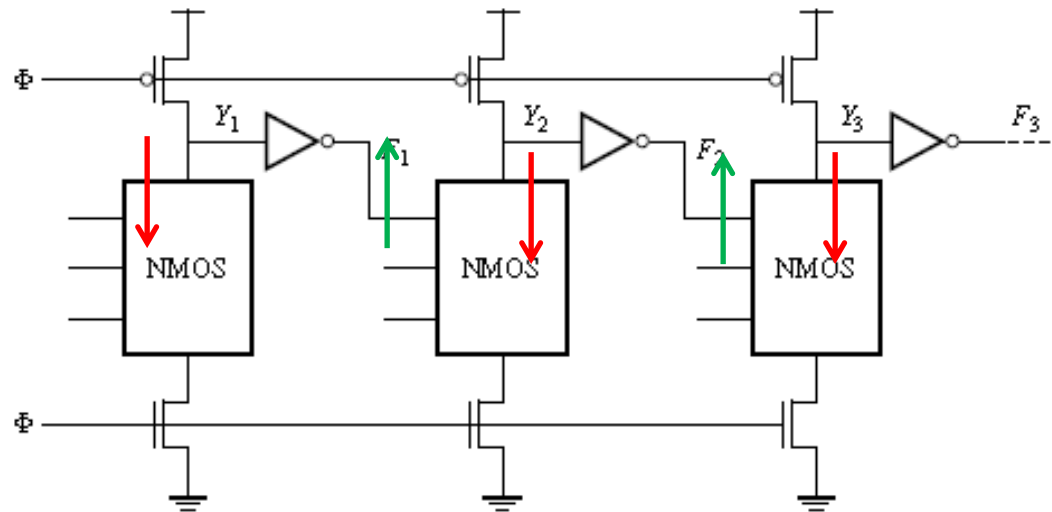


When several domino stages are put in series

The output nodes fall in order similar to domino game!
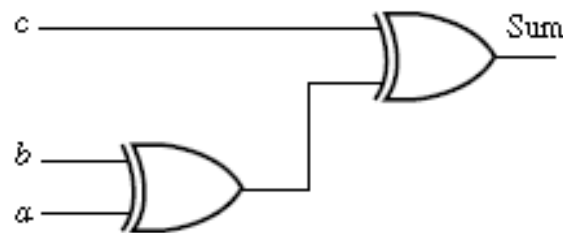
# Domino Logic - Example




Implement the function  $sum = a \oplus b \oplus c$  in domino logic. Assume that the literals  $a, \bar{a}, b, \bar{b}$  are available as stable inputs to the gates.




$$X = a \oplus b = a\bar{b} + \bar{a}b$$

$$\bar{X} = \overline{a \oplus b} = ab + \bar{a}\bar{b}$$
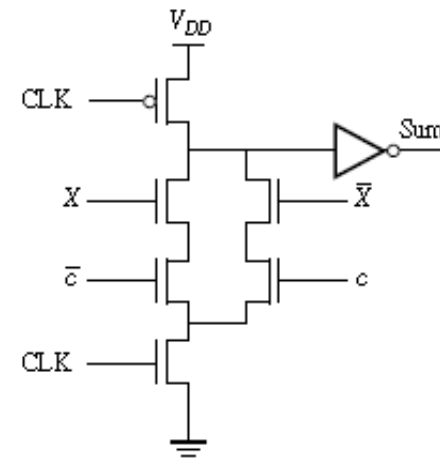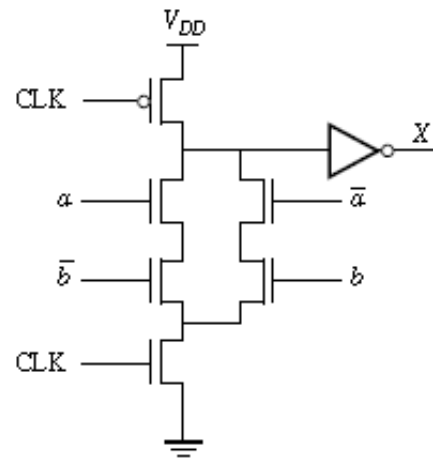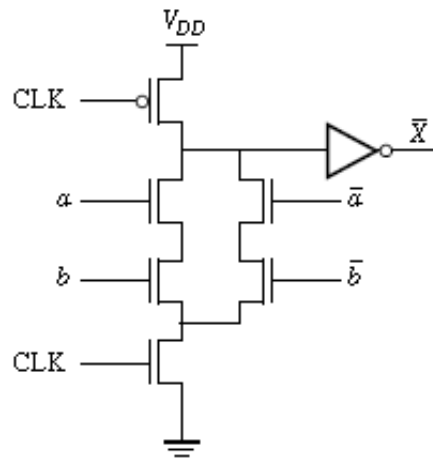
$$Sum = c \oplus X = c\bar{X} + \bar{c}X$$




# Domino Logic - issues

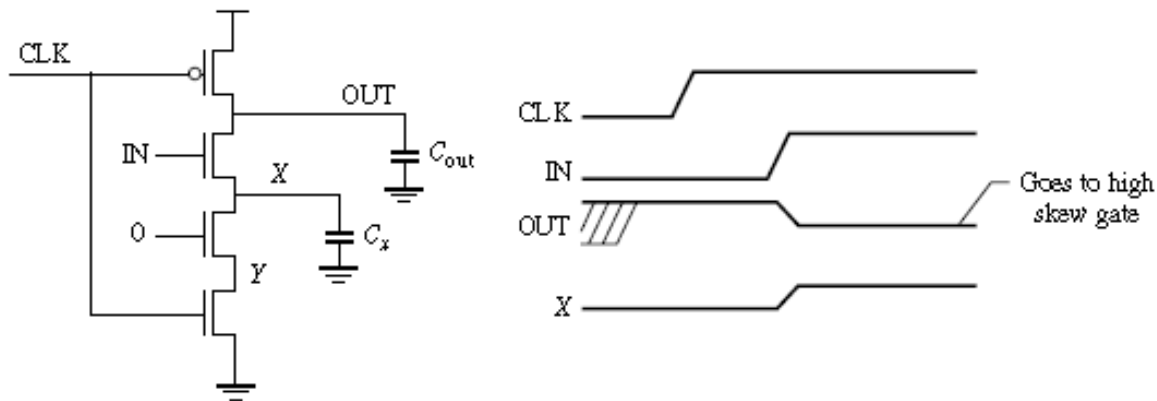

Through the evaluation phase, imagine there is no pull-down path, however, there are some On Transistors, **Charge sharing** can potentially lower the output voltage below the Threshold voltage of the subsequent inverter and fail the gate, there are several remedies

1. Increases Cap at OUT
2. skew the inverter

# Keeper cell in Domino Logic

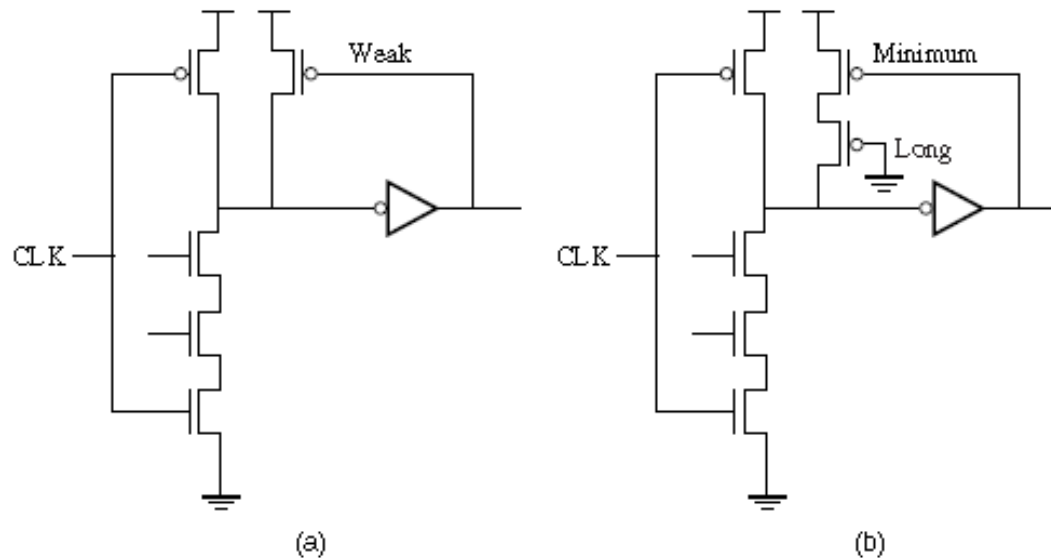


A Popular remedy is to place a weak pull-up transistor connected to the output. This will supply the required charge during the evaluation phase.

To avoid large loading on the inverter we can place two transistors in series

# Domino Logic - Example

For the domino function shown below, assume 45 nm technology parameters and answer the following questions:


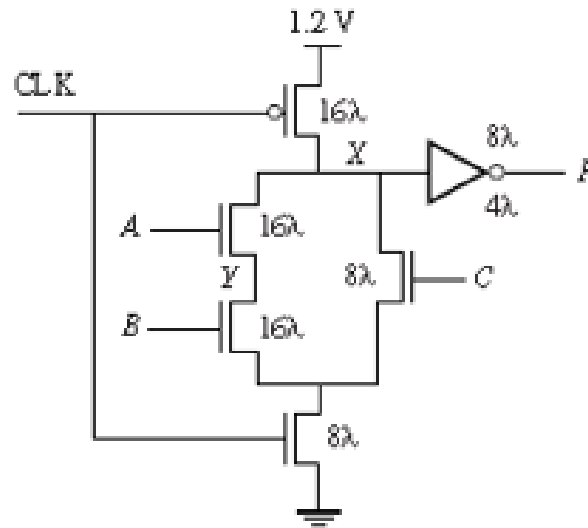
- a) What functions does the gate perform at the output F
- b) How much clock feedthrough do we observe at the internal node X? is this a potential problem?
- c) What is the worst-case charge sharing that we observe at node X?



# Domino Logic - Example



---

# Differential Domino Logic

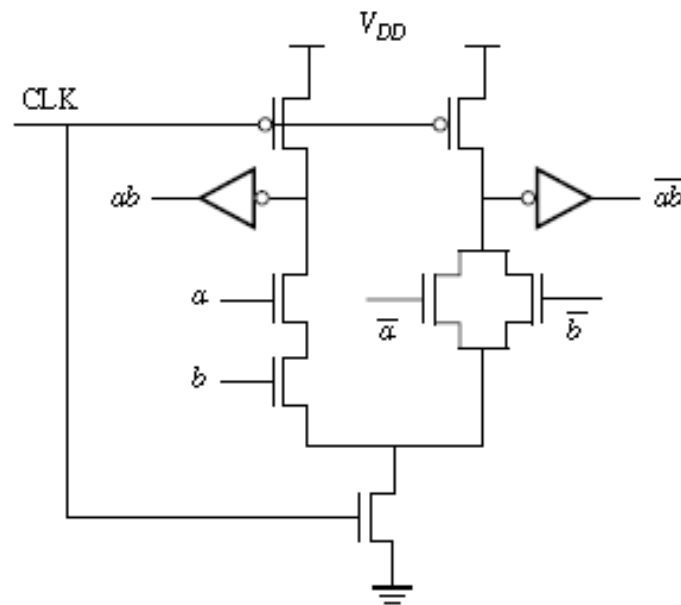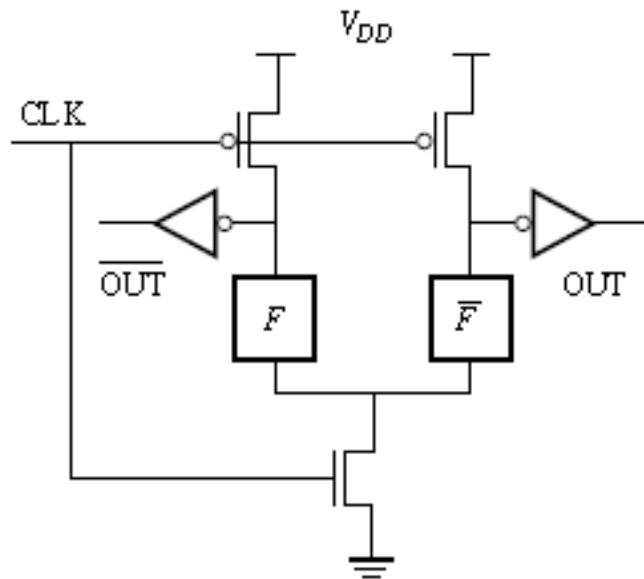

To overcome the problem of non-inverting output we can adopt the differential architecture

# Improved Differential Domino Logic

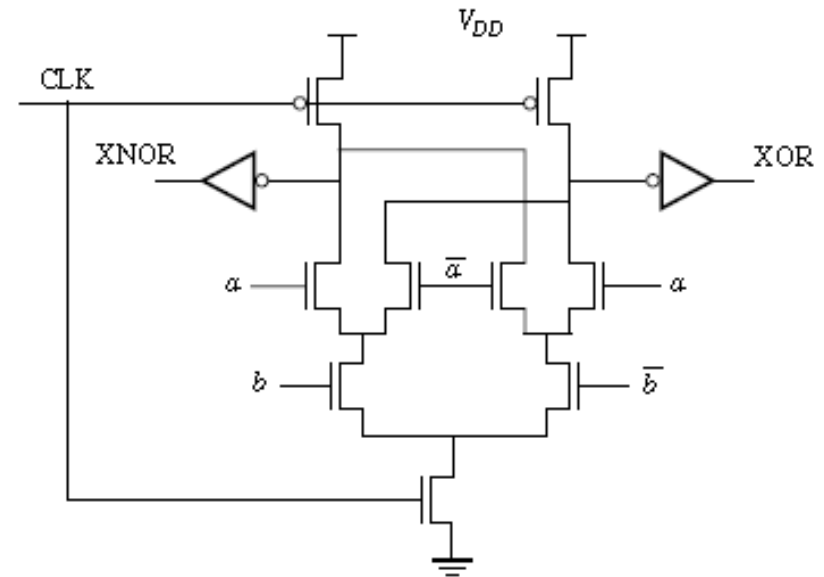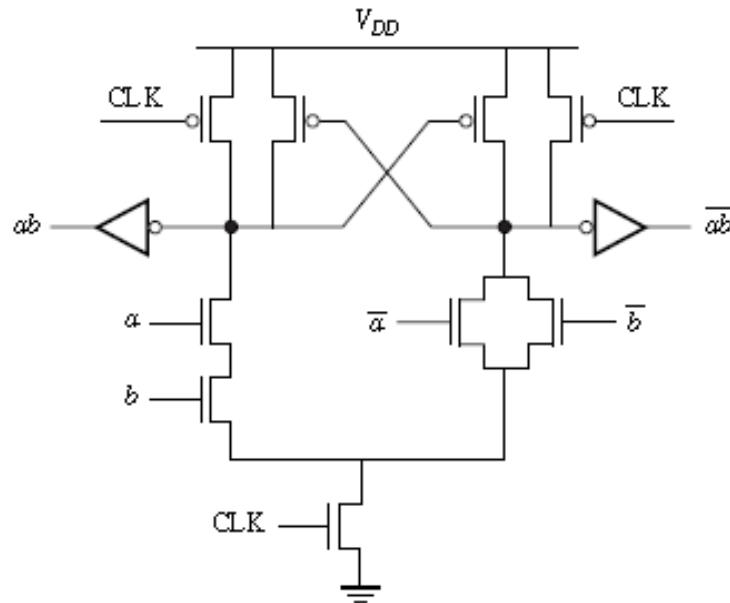

Differential Architecture helps reduce the devices for both

1. Keeper cells
2. Pull-down paths