
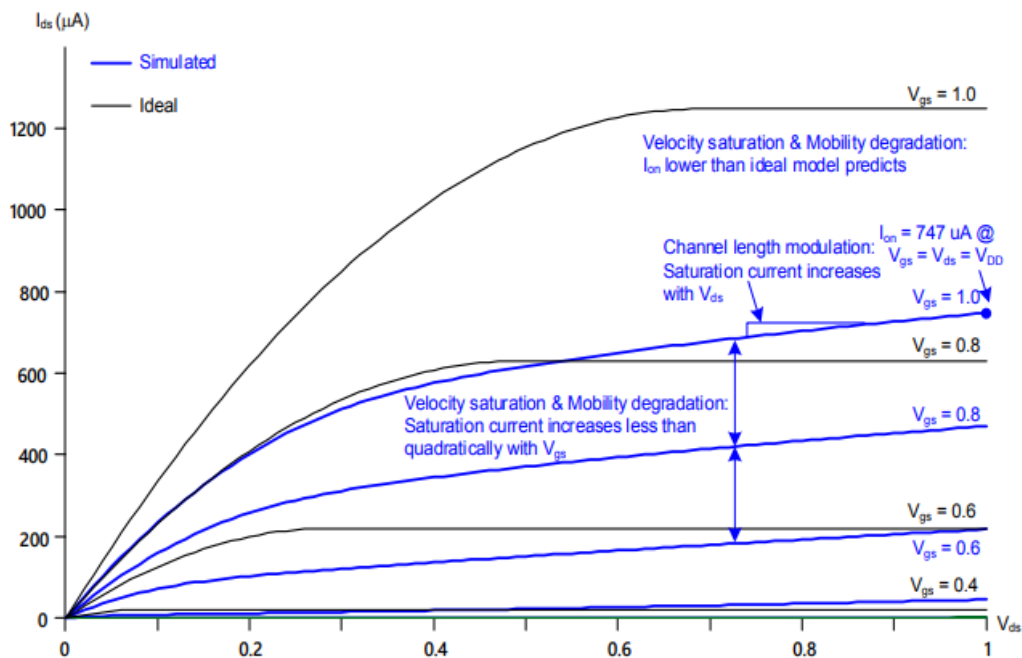


Sample Questions

 1. I-V plot for an NMOS is shown below in a 65nm CMOS process with 1V of supply. The solid curve is the ideal Shockley curve, whereas the dashed curve is from simulation. Identify the non-idealities on the plot, and list the reasons for them. [3]



The slope in saturation region is due to the extra term $(1+\lambda V_{ds})$ in saturation current expression creating a linear dependence on V_{ds}

2. (a) (4pts) What is the effect of the changing the substrate-bias voltage, V_{SB} from 0V to 1V on the following characteristics? Answer can be: increases, decreases or no change. Use $2|\phi_F| = 0.8V$ if needed.



threshold voltage, V_T : increases ☒ decreases ☐ no change ☐

source junction cap., C_J : increases ☐ decreases ☒ no change ☐

gate capacitance, C_G : increases ☐ decreases ☐ no change ☒

subthreshold current, I_{SUB} : increases ☐ decreases ☒ no change ☐

  3. (a) Compute the switching threshold of the inverter below and then sketch the voltage transfer characteristics.



$$V_S = \frac{V_{DD} - |V_{TP}| + \chi V_{TN}}{1 + \chi}$$

$$= \frac{1.2 - 0.4 + \chi(0.4)}{1 + \chi}$$


$$\chi = \sqrt{\frac{\mu_n W_n}{\mu_p W_p}} \approx 1.4$$

$$\therefore V_S \approx 0.57V$$

(b) (3pts) Re-design the inverter to produce a switching threshold of 0.6V.

$$0.6 = \frac{1.2 - 0.4 + 0.4\chi}{1 + \chi} \Rightarrow \boxed{\chi = 1}$$

 - (c) The inverter in part (a) drives 4 identical inverters as shown below. Compute t_{PHL} for the first inverter using simple hand calculations. Input is a step function.




$$t_{PHL} = (0.69) \left(\frac{12.5K}{3} \right) (0.9 pF + 4(2)(0.9) pF) = 23 ps$$

$$t_{PLH} = (0.69) \left(\frac{30K}{6} \right) (0.9 pF + 4(1.8) pF) = 28 ps$$

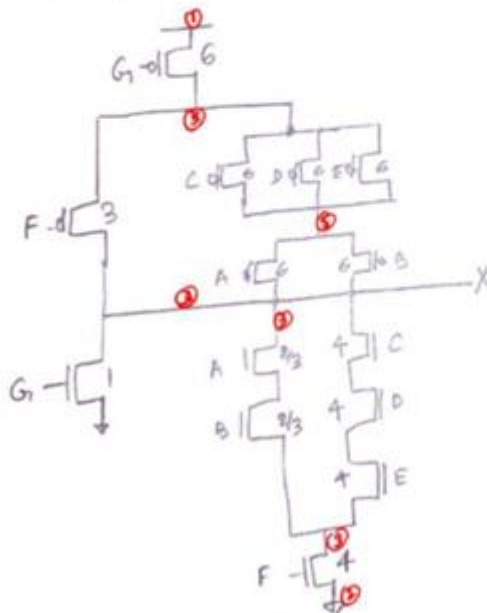4. Consider the logic function $X = ((A' + B')(C' + D' + E') + F')G'$, implemented using complementary CMOS.
- Draw the transistor level schematic.
 - Size the transistors to produce same WC delay as standard inverter

$$X = [(\bar{A} + \bar{B})(\bar{C} + \bar{D} + \bar{E}) + \bar{F}] \bar{G}$$

As each i/p is complemented, while the o/p is not, we can draw the transistor schematic by using the series-shunt connection of NMOS in PMOS!



Aliter: De-Morgan's Law

$$X = \overline{[(\bar{A} + \bar{B})(\bar{C} + \bar{D} + \bar{E}) + \bar{F}]G_1} = \overline{(\bar{A} + \bar{B})(\bar{C} + \bar{D} + \bar{E}) + \bar{F}} + G_1 = \overline{(\bar{A} + \bar{B})(\bar{C} + \bar{D} + \bar{E})} F + G_1$$

$$= (\overline{\bar{A} + \bar{B}})(\overline{\bar{C} + \bar{D} + \bar{E}}) F + G_1 = (AB + CDE) F + G_1$$

(c) Which input pattern(s) would give the worst and best equivalent HL or LH delay? [4*1=4]

① Worst case HL Pulldown: All paths have equal resistance \Rightarrow worst case charges max^m # of internal caps. Assume $F = G_1 = 0$ initially such that both pdn paths OFF.

$F = 0$; $A = B = C = D = E = 1$; $G_1: 0 \rightarrow 1 \Rightarrow$ charge on X and all internal nodes discharging through " G_1 " transistor.
internal nodes charged to VDD.

② Worst case LH pullup: ($X: 0 \rightarrow 1$)

$F = 0$; $G_1 = 1$; $A = B = C = D = E = 1$; $G_1: 1 \rightarrow 0 \Rightarrow$ G_1 must charge up internal nodes both in pu and pdn network!
all internal nodes discharged to zero

③ Best case HL Pulldown ($X: 1 \rightarrow 0$):

Make as many paths ON as possible to minimize resistance.

(G_1, A, B, C, D, E, F) all $0 \rightarrow 1$


④ Best case LH pullup ($X: 0 \rightarrow 1$)

(G_1, F, C, D, E, A, B) all $1 \rightarrow 0$

- (e) Sketch the layout (using stick diagrams) in minimum area (i.e. fewest diffusion breaks).
 [20 (Correct layouts for NMOS & PMOS – 5 each, minimum breaks – 10)]

In 2(a), as shown in red, the PMOS path has 4 odd nodes
 ⇒ will have diffusion breaks
 The NMOS path seems fine

Redrawing.

 

No diffusion break.

