

DIBL
reduces V_{th}

It is an
exponential
dependence

1) Choose the right answer (3 pts):

a) Threshold voltage increases as we increase V_{ds} in short channel devices

T

(F)

b) Pseudo NMOS design draws static current when output is low

(T)

F

c) Gate leakage quadratically increases with decreasing gate oxide thickness

T

(F)

c) What is the effect of changing the substrate bias voltage, V_{SB} from 1 V to 0 V for a MOS device. Answer either increase, decrease or no change. Estimate the percentage change if you picked "increase" or "decrease" and show your work for estimates. Use $2|\phi_F| = 0.8V$ and $\phi_B = 0.9V$ (built-in junction potential), $V_{dd} = 1.2V$ (4pts).

a) Source junction cap, C_j increase by 45% decrease by ____% no change

b) Threshold voltage, V_{th} : increase by ____% decrease by 18% no change

$$a) C_j = \frac{C_{j0} A}{(1 - \frac{V_J}{\phi_B})^{1/2}} \Rightarrow \frac{C_{j2}}{C_{j1}} = \sqrt{\frac{(1 - V_{J2}/\phi_B)}{(1 - V_{J1}/\phi_B)}}$$

$$V_{SB} = 0 \Rightarrow V_J = 0$$

$$V_{SB} = 1 \Rightarrow V_J = -1$$

* V_J is forward bias
Voltage

$$\frac{C_{j2}(V_{SB}=0)}{C_{j1}(V_{SB}=1)} = \sqrt{\frac{(1 - (-1)/0.9)}{1}} \approx 1.45 \Rightarrow 45\% \text{ increase}$$


$$b) V_T = V_{T0} + \gamma (\sqrt{V_{SB} + 2\phi_F} - \sqrt{2\phi_F})$$

$$V_{T1} = 0.4 + 0.2 (\sqrt{1 + 0.8} - \sqrt{0.8}) = 0.49V$$


$$V_{T2} = V_{T0} = 0.4V$$

$$\frac{V_{T2}}{V_{T1}} = \frac{0.4}{0.49} = 0.82 \Rightarrow 18\% \text{ decrease}$$

 2. Which of the following two circuits switches faster as the input toggles? And Why (one sentence only) (2 points)



 
more current when switching
(smaller V_T)



using $V_T \uparrow$
formula

b) What is the function implemented by the following circuit (after the inverter) (3 pts)
size transistors to achieve the minimum delay (4 pts)

WC PD

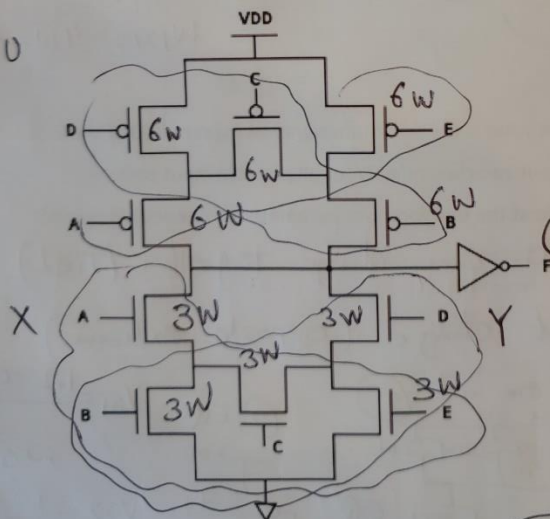

Since there is an inverter
we can simply
find PD & declare
as F

method 1

$$X = A \cdot (B + CE)$$

$$Y = D \cdot (E + BC)$$

$$F = X + Y = A \cdot (B + CE) + D(E + BC)$$

method 2

if $C = 0$ (NMOS OFF)

$$PD \Rightarrow AB + DE$$

if $C = 1$ (NMOS ON)

$$PD \Rightarrow (A + D) \cdot (B + E)$$



WC PD or PD is 3 transistor

$$SO, F = \overline{C}(AB + DE) + C(A + D)(B + E)$$


Combine

A

  3. The following pictures show SR-latch implementation using NOR gates (and truth table just for your reference). Design the size of devices (i.e. Widths of transistors) in NOR to deliver a worst-case delay of 400 ps from S to Q in a 90 nm technology (you can assume $L = 100\text{nm}$ for simplicity). Assume there is an external capacitance of 200 fF attached to both Q and \bar{Q} which dominates capacitance, i.e. you can ignore device capacitance. (6 points)



 S-Q delay goes through two NOR gates so each delay $\frac{400\text{ps}}{2} = 200\text{ps}$



S	R	Q	\bar{Q}
0	0	Q	\bar{Q}
0	1	0	1
1	0	1	0
1	1	0	0


$$T_{PHL} = T_{PLH} = 0.7RC = 200\text{ps}$$

$$= 0.7 \times 200\text{fF} \times R = 200\text{ps}$$

$$= 0.7 \times 200 \times 10^{-15} \times \frac{100\text{nm}}{W} = 200\text{ps}$$

$$W = 1050\text{nm} = 1.05\mu\text{m}$$


$$W_{PMOS} = 4W = 4.2\mu\text{m}$$

 


b) Assuming a noise-free environment what is the minimum signal swing required at the input of a 3-input NAND gate to ensure the output switches reliably for all possible input pattern combinations ($W_n = 300\text{nm}$, use table at the end for more parameters if needed) (4 points)

- ① For a NAND3 All inputs can change together (Tied) one extreme
or
② only one input change (opposite extreme)


inputs tied

 


① EQ

 
 
$$X_1 = \sqrt{\frac{24 \times W}{6 \times 6W}} \sim 0.82$$



② EQ

 


$$X_2 = \sqrt{\frac{24 \times 3W}{6 \times 2W}} \sim 2.45$$

$$V_{S1} = \frac{1.2 - 0.4 + 0.82 \times 0.4}{1 + 0.82} \sim 0.62\text{V}$$


$$V_{S2} = \frac{1.2 - 0.4 + 2.45 \times 0.4}{1 + 2.45} \sim 0.51\text{V}$$

$$\Delta V_S \sim 110\text{mV}$$

 Input should have at least 110mV swing to span V_S variation



 4. Implement the function $A(B+D)+C\bar{A}$ using CMOS static logic to minimize worst-case delay knowing that input "C" is the latest arriving signal and show the stick diagram layout (no break in diffusion - no sizing required)(6pts).



$$F = A(B+D) + C\bar{A}$$



$$\bar{F} = \overline{A(B+D) + C\bar{A}}$$

$$= (\bar{A} + \bar{B}\bar{D}) \cdot (\bar{A} + \bar{C})$$


← C late arrival, keep it close to the output

One Euler path is

$$A\bar{C}\bar{A}\bar{D}\bar{B}$$

  


 There are other possible Euler path such as $\bar{A}\bar{C}\bar{A}\bar{B}\bar{D}$, etc...



$$N=5$$

 5. If the rise and fall propagation delay for the inverters in the following figure are different and denoted by T_{PHL} and T_{PLH} , respectively, what is the frequency of oscillation for the ring oscillator with "N" inverters in the loop? (3pts)




It has to go through the loop twice to get to original state

$$\text{so } T_D = 5T_{PHL} + 5T_{PLH}$$

$$f = \frac{1}{5T_{PLH} + 5T_{PHL}} = \frac{1}{N(T_{PLH} + T_{PHL})}$$

 Calculate the frequency of oscillation if each inverter is built as shown below (6pts).



$$R_{PD} = R_{eq} \times \frac{L}{W} = 15\text{K}\Omega \times \frac{0.1}{1} = 1.5\text{K}\Omega$$

$$R_{PU} = R_{eq} \times \frac{L}{W} = 30\text{K}\Omega \times \frac{0.1}{0.4} = 7.5\text{K}\Omega$$

$$C_{tot} = C_{eff} \times (W_N + W_P) + C_g \times W_N$$

$$= 1\text{fF}/\mu\text{m} \left(\overbrace{1}^{\text{NMOS}} + \overbrace{0.4}^{\text{PMOS}} \right) + 2\text{fF}/\mu\text{m} (1\mu\text{m})$$

each inverter only drives an NMOS

$$= 3.4\text{fF}$$

NO 0.7 required because circuit is self driving, it is ramp input, no external source

$$T_{PHL} = 1.5\text{K}\Omega \times 3.4\text{fF} = 5.1\text{ps}$$

$$T_{PLH} = 7.5\text{K}\Omega \times 3.4\text{fF} = 25.5\text{ps}$$

$$f = \frac{1}{5(5.1\text{ps} + 25.5\text{ps})} \approx \underline{\underline{6.53\text{GHz}}}$$

